

1. A1

$$R = 10^3 \Omega$$

$$C = 1 \mu\text{F}$$

$$U_0 = 5\text{V}$$

$$U_m = 10\text{V}$$

$$\omega = 1000 \text{ s}^{-1}$$

$$\varphi = \frac{\pi}{4}$$

$$u(t) = U_0 + U_m \cdot \sin(\omega t + \varphi)$$

$$u(t) = 5 + 10 \sin\left(1000t + \frac{\pi}{4}\right)$$

$$U_m = 10 e^{j\frac{\pi}{4}} \text{ V}$$

$$Z = R + \frac{1}{j\omega C} = 10^3 + \frac{1}{j \cdot 10^3 \cdot 10^{-6}} = 1000(1 - j) = 1414 e^{-j\frac{\pi}{4}} \Omega$$

$$U = Z \cdot I$$

$$\hat{I}_m = \frac{\hat{U}_m}{Z} = \frac{10 e^{j\frac{\pi}{4}}}{1414 e^{-j\frac{\pi}{4}}} = 7,071 \cdot 10^{-3} e^{j1,5707} \text{ A}$$

$$i(t) = 7,071 \cdot 10^{-3} \cdot (1000 + 1,5707) \text{ A}$$

1. A2

$$R = 1 \text{ k}\Omega$$

$$\varphi = \frac{\pi}{4}$$

$$L = 1 \text{ H}$$

$$U_0 = 5\text{V}$$

$$U_m = 10\text{V}$$

$$\omega = 10^3 \text{ s}^{-1}$$

$$u(t) = U_0 + U_m \cdot \sin(\omega t + \varphi)$$

$$u(t) = 5 + 10 \cdot \sin\left(10^3 t + \frac{\pi}{4}\right)$$

$$\hat{U}_m = 10 e^{j\frac{\pi}{4}}$$

$$Z = R + L = R + j\omega L = 10^3 + j \cdot 10^3 \cdot 1 =$$


$$= 10^3 \cdot (1 + j) = 1414,213 e^{j0,785} \Omega$$

$$I = \frac{U}{Z}$$

$$\hat{I}_m = \frac{\hat{U}_m}{Z} = \frac{10 e^{j\frac{\pi}{4}}}{1414,213 e^{j0,785}} = 7,071 \cdot 10^{-3} \text{ A}$$

$$i(t) = \frac{U_0}{R} + \hat{I}_m \sin(\omega t) = \left[\frac{5}{1000} + 7,071 \cdot 10^{-3} \sin(10^3 t) \right] \text{ A}$$

1A3

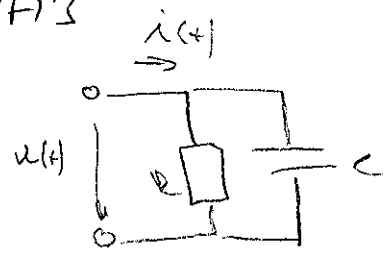

$R = 1 \text{ k}\Omega$
 $C = 1 \mu\text{F}$
 $U_0 = 5 \text{ V}$
 $U_{m1} = 10 \text{ V}$
 $\omega = 10^3 \text{ s}^{-1}$
 $\varphi = \frac{\pi}{4}$

$u(t) = U_0 + U_{m1} \sin(\omega t + \varphi)$
 $u(t) = 5 + 10 \sin(10^3 t + \frac{\pi}{4})$
 $U_{m1} = 10 e^{j\frac{\pi}{4}} \text{ V}$


$$Z = \frac{R \cdot C}{R + C} = \frac{R \cdot \frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} = \frac{R}{j\omega C R + 1} = \frac{R}{j\omega C R + 1}$$

$$= \frac{10^3}{j \cdot 10^3 \cdot 10^{-6} \cdot 10^3 + 1} = \frac{10^3}{j + 1} = 500 - 500j = 707,106 e^{-j\frac{\pi}{4}} \Omega$$

$$\vec{I}_m = \frac{U}{Z} \Rightarrow \vec{I}_m = \frac{U_m}{Z} = \frac{10 e^{j\frac{\pi}{4}}}{500 - 500j} = 14,1421 \cdot 10^{-3} e^{j1,1071} \text{ A}$$

$$i(t) = \frac{U_0}{R} + \vec{I}_m \sin(\omega t + \varphi) = \left[5 \cdot 10^{-3} + 14,1421 \cdot 10^{-3} \sin(10^3 t + 1,1071) \right] \text{ A}$$

1A4

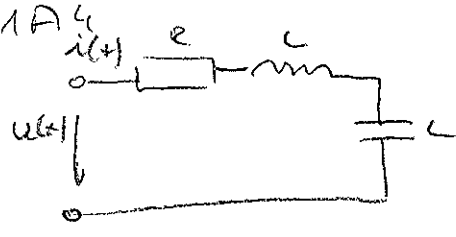

$R = 10^3 \Omega$
 $L = 1 \text{ H}$
 $C = 10^{-6} \text{ F}$
 $U_0 = 5 \text{ V}$
 $U_{m1} = 10 \text{ V}$
 $\omega = 2 \cdot 10^3 \text{ s}^{-1}$
 $\varphi = \frac{\pi}{4}$


$u(t) = U_0 + U_{m1} \sin(\omega t + \varphi) =$
 $= 5 + 10 \sin(2 \cdot 10^3 t + \frac{\pi}{4})$
 $U_{m1} = 10 e^{j\frac{\pi}{4}}$

$$Z = R + C + L = R + j\omega L + \frac{1}{j\omega C} = 10^3 + j2 \cdot 10^3 \cdot 1 + \frac{1}{j \cdot 2 \cdot 10^3 \cdot 10^{-6}} = 1000 + 1500j - 500j = 1000 + 1000j = 1414,21 e^{j0,7071} \Omega$$

$$\vec{I}_m = \frac{U_m}{Z} = \frac{10 e^{j\frac{\pi}{4}}}{1414,21 e^{j0,7071}} = 7,071 \cdot 10^{-3} e^{-j0,1979} \text{ A}$$

$$i(t) = \left[5,7071 \cdot 10^{-3} \sin(2 \cdot 10^3 t - 0,1979) \right] \text{ A}$$

1B1

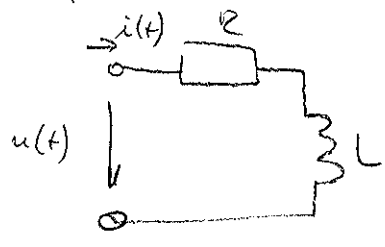

$R = 10^3 \Omega$
 $L = 1 \text{ H}$
 $\bar{I}_0 = 10 \text{ mA}$
 $\bar{I}_{\text{imp}} = 5 \text{ mA}$
 $\omega = 10^3 \text{ s}^{-1}$
 $\varphi = \frac{1}{4}\pi$


$i(t) = \bar{I}_0 + \bar{I}_{\text{imp}} \cdot \sin(\omega t + \varphi)$
 $i(t) = 10^{-2} + 5 \cdot 10^{-3} \cdot \sin(10^3 t + \frac{1}{4}\pi)$
 $\bar{I}_{\text{m}} = 5 \cdot 10^{-3} e^{j\frac{1}{4}\pi}$

$Z = R + L = R + j\omega L = 1000 \cdot (1 + j) = 1414,213 e^{j\frac{1}{4}\pi} \Omega$

$\hat{U} = Z \cdot \hat{I} \rightarrow \hat{U}_{\text{m}} = Z \cdot \hat{I}_{\text{m}} = 1414,213 e^{j\frac{1}{4}\pi} \cdot 5 \cdot 10^{-3} e^{-j\frac{1}{4}\pi} = 7,071 e^{j\frac{1}{2}\pi}$

$u(t) = R \cdot \bar{I}_0 + \hat{U}_{\text{m}} = 10 + 7,071 \cdot \sin(10^3 t + \frac{1}{2}\pi) \text{ V}$

1B2

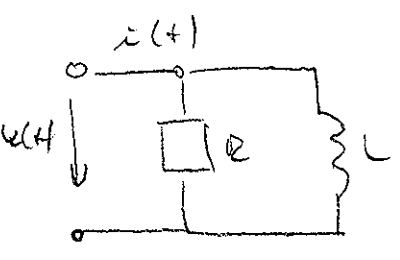

$R = 10^3 \Omega$
 $L = 1 \text{ H}$
 $\bar{I}_0 = 10 \text{ mA}$
 $\bar{I} = 5 \text{ mA}$
 $\omega = 10^3 \text{ s}^{-1}$
 $\varphi = \frac{\pi}{4}$


$i(t) = \bar{I}_0 + \bar{I}_{\text{m}} \cdot \sin(\omega t + \varphi) =$
 $= 10^{-2} + 5 \cdot 10^{-3} \cdot \sin(10^3 t + \frac{1}{4}\pi)$
 $\bar{I}_{\text{m}} = 5 \cdot 10^{-3} e^{j\frac{1}{4}\pi} \text{ A}$

$Z = \frac{R \cdot L}{R + L} = \frac{R \cdot j\omega L}{R + j\omega L} = \frac{10^3 \cdot j \cdot 10^3 \cdot 1}{10^3 + j \cdot 10^3 \cdot 1} = \frac{10^6 j}{10^3 (1 + j)}$
 $= 100 + 100j = 707,106 e^{j\frac{1}{4}\pi} \Omega$

$\hat{U}_{\text{m}} = Z \cdot \hat{I}_{\text{m}} = 707,106 e^{j\frac{1}{4}\pi} \cdot 5 \cdot 10^{-3} e^{j\frac{1}{4}\pi} = 3,53553 e^{j\frac{1}{2}\pi} \text{ V}$

$u(t) = 3,53553 \cdot \sin(10^3 t + \frac{1}{2}\pi) \text{ V}$

133

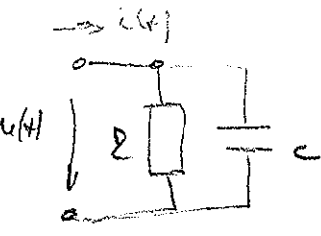

$R = 10^3 \Omega$
 $C = 10^{-6} F$
 $I_0 = 10 \mu A$
 $I_m = 5 \mu A$
 $\omega = 10^3 s^{-1}$

$\varphi = \frac{\pi}{4}$


$i(t) = I_0 + I_m \sin(\omega t + \varphi) =$
 $10^{-2} + 5 \cdot 10^{-3} \sin(10^3 t + \frac{\pi}{4})$
 $\hat{I}_m = 5 \cdot 10^{-3} e^{j \frac{\pi}{4}}$

$Z = \frac{R \cdot C}{R + C} = \frac{R \cdot \frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} = \frac{R}{j\omega C + 1} = \frac{R}{j\omega C}$
 $= \frac{10^3}{j \cdot 10^3 \cdot 10^{-6} + 1} = \frac{10^3}{j + 1} = 500 - 500j = 707,106 e^{-j \frac{\pi}{4}} \Omega$

$\hat{U}_m = Z \cdot \hat{I}_m = 707,106 e^{-j \frac{\pi}{4}} \cdot 5 \cdot 10^{-3} e^{j \frac{\pi}{4}} = 3,5355 V$

$i(t) = \frac{I_0}{R} + \hat{U}_m \sin(\omega t + \varphi) = 10 + 3,5355 \sin(10^3 t) V$

134

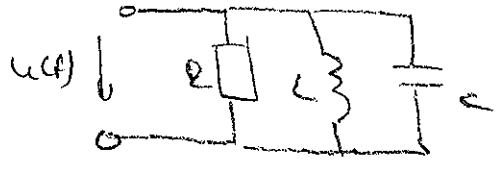

$R = 10^3 \Omega$
 $L = 1 H$
 $C = 10^{-6} F$
 $I_0 = 10 \mu A$
 $I_m = 5 \mu A$
 $\omega = 2 \cdot 10^3 s^{-1}$

$\varphi = \frac{\pi}{4}$

$i(t) = I_0 + I_m \sin(\omega t + \varphi)$
 $i(t) = 10^{-2} + 5 \cdot 10^{-3} \sin(2 \cdot 10^3 t + \frac{\pi}{4}) A$
 $\hat{I}_m = 5 \cdot 10^{-3} e^{j \frac{\pi}{4}} A$


$Z = \left(\frac{1}{R} + \frac{1}{L} + \frac{1}{C} \right)^{-1} = \left(\frac{LC + RC + LR}{R \cdot L \cdot C} \right)^{-1} = \frac{R \cdot L \cdot C}{LC + RC + LR}$

$= \frac{10^3 \cdot j\omega L \cdot 1}{j\omega C} = \frac{j\omega L}{j\omega C} + \frac{R}{j\omega C} + \frac{j\omega L \cdot R \cdot j\omega C}{j\omega C}$
 $= \frac{10^3 \cdot j \cdot 2 \cdot 10^3 \cdot 1}{j \cdot 2 \cdot 10^3 \cdot 1 + 10^3 + (-1) \cdot (2 \cdot 10^3)^2 \cdot 10^{-6}}$
 $= \frac{2 \cdot 10^6 j}{-3000 + 2000j} = \sqrt{54,7001} e^{-j 0,982} \Omega$

$\hat{U}_m = \hat{I}_m \cdot Z = 5 \cdot 10^{-3} e^{j \frac{\pi}{4}} \cdot \sqrt{54,7001} e^{-j 0,982} = 2,7735 e^{-j 0,1973} V$

$i(t) = 2,7735 \sin(2 \cdot 10^3 t - 0,1973) V$

1C1

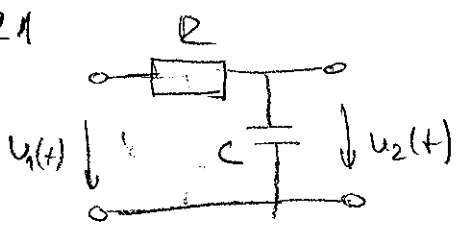


$R = 10^3 \Omega$
 $C = 10^{-6} F$
 $U_0 = 5V$
 $U_{m1} = 10V$
 $\omega = 10^3 s^{-1}$
 $\varphi = \frac{\pi}{4}$

$u(t) = U_0 + U_m \sin(\omega t + \varphi)$
 $u(t) = 5 + 10 \sin(10^3 t + \frac{\pi}{4})$
 $\hat{U}_m = 10 e^{j \frac{\pi}{4}} V$

$$\hat{U}_{2m} = \frac{\hat{U}_{1m} \cdot C}{R + C} = \frac{\hat{U}_{1m}}{j\omega C} = \frac{\hat{U}_{1m}}{j\omega RC + 1} = \frac{10 e^{j \frac{\pi}{4}}}{j \cdot 10^3 \cdot 10^3 \cdot 10^{-6} + 1} = \frac{10 e^{j \frac{\pi}{4}}}{j + 1} = \sqrt{10} = 7,071 V$$

$u_2(t) = U_0 + U_{2m} \sin(\omega t + \varphi) = 5 + 7,071 \sin(10^3 t) V$

1C2

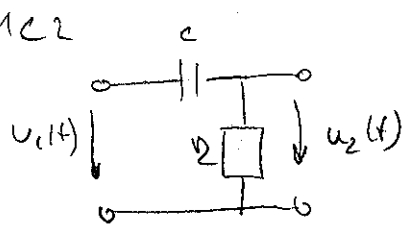


$R = 10^3 \Omega$
 $C = 10^{-6} F$
 $U_0 = 5V$
 $U_m = 10V$
 $\omega = 10^3 s^{-1}$
 $\varphi = \frac{\pi}{4}$

$u(t) = U_0 + U_m \sin(\omega t + \varphi)$
 $u(t) = 5 + 10 \sin(10^3 t + \frac{\pi}{4})$
 $\hat{U}_{m1} = 10 e^{j \frac{\pi}{4}} V$

$$\hat{U}_{m2} = \frac{\hat{U}_{m1} \cdot R}{R + C} = \frac{\hat{U}_{m1} \cdot R}{R + \frac{1}{j\omega C}} = \frac{10 e^{j \frac{\pi}{4}} \cdot 10^3}{10^3 + \frac{1}{j \cdot 10^3 \cdot 10^{-6}}} = 7,071 e^{j \frac{\pi}{2}} V$$

$u_2(t) = 7,071 \sin(10^3 t + \frac{\pi}{2}) V$

1C3

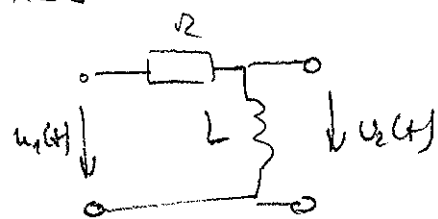

$$R = 10^3 \Omega$$

$$L = 1 \text{ H}$$

$$U_0 = 7 \text{ V}$$

$$U_m = 10 \text{ V}$$

$$\omega = 10^3 \text{ s}^{-1}$$

$$\varphi = \frac{\pi}{4}$$

$$u(t) = U_0 + U_m \cdot \sin(\omega t + \varphi)$$

$$= 7 + 10 \cdot \sin(10^3 t + \frac{\pi}{4})$$


$$\hat{U}_m = 10 e^{j \frac{\pi}{4}} \text{ V}$$

$$\hat{U}_{2m} = \frac{\hat{U}_{1m} \cdot L}{R + L} = \frac{\hat{U}_{1m} \cdot j\omega L}{R + j\omega L} = \frac{10 \cdot e^{j \frac{\pi}{4}} \cdot j \cdot 10^3 \cdot 1}{10^3 + j \cdot 10^3 \cdot 1} =$$

$$= 7,071 e^{j \frac{\pi}{2}} \text{ V}$$

$$u_2(t) = 7,071 \sin(10^3 t + \frac{\pi}{2}) \text{ V}$$

1C4

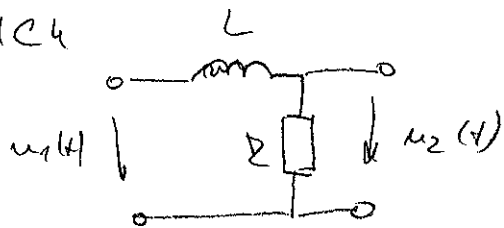

$$R = 10^3 \Omega$$

$$L = 1 \text{ H}$$

$$U_0 = 7 \text{ V}$$

$$U_m = 10 \text{ V}$$

$$\varphi = \frac{\pi}{4}$$

$$\omega = 10^3 \text{ s}^{-1}$$

$$u(t) = U_0 + U_m \cdot \sin(\omega t + \varphi)$$

$$u(t) = 7 + 10 \sin(10^3 t + \frac{\pi}{4})$$


$$\hat{U}_{m1} = 10 e^{j \frac{\pi}{4}} \text{ V}$$

$$\hat{U}_{2m} = \frac{\hat{U}_{1m} \cdot R}{L + R} = \frac{\hat{U}_{1m} \cdot R}{j\omega L + R} = \frac{10 e^{j \frac{\pi}{4}} \cdot 10^3 \cdot 1}{j \cdot 10^3 \cdot 1 + 10^3} =$$

$$= 7,071 \text{ V}$$

$$u_2(t) = 7 + 7,071 \cdot \sin(10^3 t) \text{ V}$$

1C5

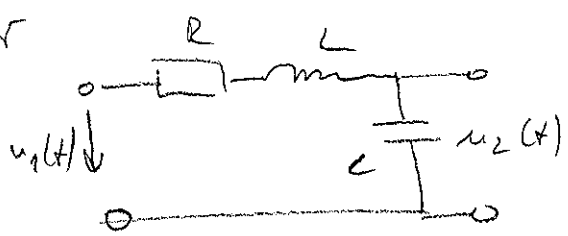


$R = 10^3 \Omega$
 $L = 14$
 $C = 10^{-6} F$
 $U_0 = 5V$
 $U_{m1} = 10V$
 $\varphi = \frac{\pi}{4}$; $\omega = 10^3 s^{-1}$

$u(t) = U_0 + U_m \cdot \sin(\omega t + \varphi)$
 $u(t) = 5 + 10 \cdot \sin(10^3 t + \frac{\pi}{4})$
 $\hat{U}_{m1} = 10 e^{j\frac{\pi}{4}} V$

$$\hat{U}_{m2} = \frac{U_{m1} \cdot C}{L + R + C} = \frac{\frac{U_{m1}}{j\omega L}}{j\omega L + R + \frac{1}{j\omega C}} = \frac{\hat{U}_{m1}}{j^2 \omega^2 LC + j\omega RC + 1}$$

$$= \frac{10 e^{j\frac{\pi}{4}}}{j^2 \cdot (10^3)^2 \cdot 1 \cdot 10^{-6} + j \cdot 10^3 \cdot 10^3 \cdot 10^{-6} + 1} = \frac{10 e^{j\frac{\pi}{4}}}{-1 + j + 1} = \frac{10 e^{j\frac{\pi}{4}}}{j} = 10 e^{-j\frac{\pi}{4}} V \Rightarrow u_2(t) = 5 + 10 \cdot \sin(10^3 t - \frac{\pi}{4}) V$$

1C6

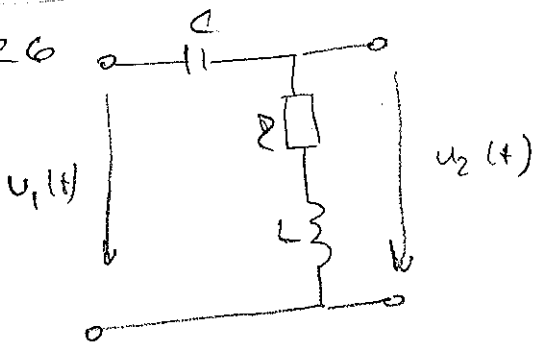


$R = 10^3 \Omega$
 $C = 10^{-6} F$
 $L = 14$
 $U_0 = 5V$
 $U_{m1} = 10V$
 $\varphi = \frac{\pi}{4}$; $\omega = 10^3 s^{-1}$

$U_1(t) = U_0 + U_m \cdot \sin(\omega t + \varphi)$
 $u_1(t) = 5 + 10 \cdot \sin(10^3 t + \frac{\pi}{4})$
 $\hat{U}_{m1} = 10 e^{j\frac{\pi}{4}} V$

$$\hat{U}_{2m} = \frac{U_{m1} \cdot (R + L)}{R + L + C} = \frac{U_{m1} \cdot (R + j\omega L)}{R + j\omega L + \frac{1}{j\omega C}}$$

$$= \frac{10 e^{j\frac{\pi}{4}} \cdot (10^3 + j \cdot 10^3 \cdot 1)}{10^3 + j \cdot 10^3 \cdot 1 + \frac{1}{j \cdot 10^3 \cdot 10^{-6}}} = 14,142 e^{j\frac{\pi}{2}} V$$
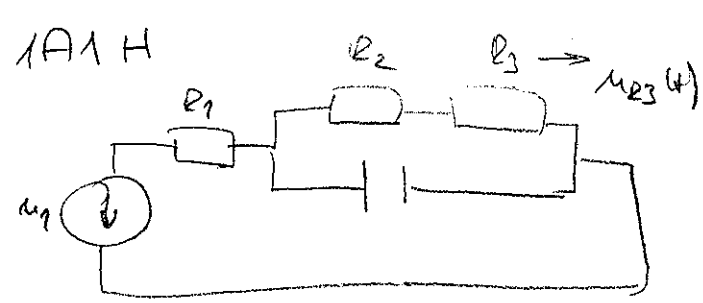
$$u_2(t) = 14,142 \sin(10^3 t + \frac{\pi}{2}) V$$



$$R_1 = 10^3 \Omega$$

$$R_2 = 2 \cdot 10^3 \Omega$$

$$R_3 = 4 \cdot 10^3 \Omega$$

$$C = 10^{-6} \text{ F}$$

$$U_0 = 5 \text{ V}; U_{1m} = 10 \text{ V}; U_{3m} = 2 \text{ V}$$

$$\omega = 10^3$$

$$\varphi_1 = \frac{\pi}{4}$$

$$\varphi_2 = -\frac{\pi}{3}$$

$$u_1(t) = U_0 + U_{1m} \sin(\omega t + \varphi_1) + U_{3m} \sin(\omega t + \varphi_2) =$$

$$= 5 + 10 \cdot \sin\left(10^3 t + \frac{\pi}{4}\right) + 2 \cdot \sin\left(10^3 t + \frac{\pi}{3}\right) \rightarrow$$

$$\hat{U}_{1m} = 10 e^{j\frac{\pi}{4}}$$

$$\hat{U}_{3m} = 2 e^{-j\frac{\pi}{3}}$$

$$\hat{U}_{02} = \frac{\hat{U}_0 \cdot R_3}{R_1 + R_2 + R_3} = \frac{5 \cdot 4 \cdot 10^3}{7 \cdot 10^3} = \frac{20}{7} \text{ V}$$

(C-parallel hat pi ss)

$$\hat{z}_{23C} = \frac{(R_2 + R_3) \cdot C}{(R_2 + R_3 + C)} = \frac{1}{\frac{1}{R_2 + R_3} + j\omega C} = \frac{R_2 + R_3}{j\omega C(R_2 + R_3) + 1} = 386,393 e^{j140^\circ} \Omega$$

$$\hat{U}_u = \left(\frac{\hat{U}_0 \cdot \hat{z}_{23C}}{R_1 + \hat{z}_{23C}} \right) \cdot \frac{R_3}{R_2 + R_3} = U_0 \cdot \left(\frac{386,393 e^{j140^\circ}}{10^3 + 386,393 e^{j140^\circ}} \right) \cdot \frac{4 \cdot 10^3}{6 \cdot 10^3} \Rightarrow$$

$$\Rightarrow \hat{U}_{1m} = 4,337 e^{j90,77^\circ}$$

$$\hat{U}_{3m} = 0,4142 e^{-j2,247^\circ}$$


($\hat{z}_{23C} - j\omega C \Rightarrow \hat{z}_{23C} = 372,820 e^{-j140^\circ}$)

$$u(t) = \hat{U}_{02} + \hat{U}_{1m} + \hat{U}_{3m}$$

$$u(t) = 2,857 + 4,337 \sin(10^3 t + 90,77^\circ) + 0,4142 \sin(10^3 t - 2,247^\circ) \text{ V}$$

$$U_{2eff} = \sqrt{\frac{U_0^2}{2} + \frac{U_{1m}^2}{2} + \frac{U_{3m}^2}{2}} = \sqrt{2,857^2 + \frac{4,337^2}{2} + \frac{0,4142^2}{2}} = 4,201 \text{ V}$$

108 H

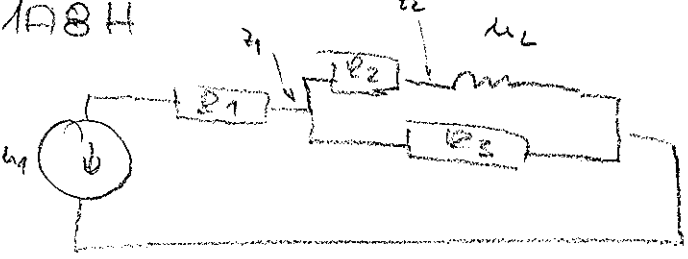

- $R_1 = 10^3 \Omega$
- $R_2 = 2 \cdot 10^3 \Omega$
- $R_3 = 4 \cdot 10^3 \Omega$
- $L = 1H$
- $U_0 = 5V$
- $U_{1m} = 10V$
- $U_{2m} = 2V$

$$\omega_0 = 10^3 \text{ s}^{-1}$$

$$\varphi_1 = \frac{\pi}{4}$$

$$\varphi_2 = -\frac{\pi}{3}$$

$$u_1(t) = 5 + 10 \sin\left(10^3 t + \frac{\pi}{4}\right) + 2 \sin\left(3 \cdot 10^3 t - \frac{\pi}{3}\right)$$

$$\hat{U}_0 = 5V \quad \hat{U}_{1m} = 10 e^{j\frac{\pi}{4}} \quad \hat{U}_{2m} = 2 e^{-j\frac{\pi}{3}}$$

$$\omega_1 = 10^3$$

$$\omega_2 = 3 \cdot 10^3$$

$\hat{U}_{0L} = 0$ - L r SS je razpojeno

$$z_{1L} = \frac{(R_2 + j\omega L) \cdot R_3}{R_2 + R_3 + j\omega L}$$

$$\omega_1 = 1470,429 e^{j0,298} \Omega \quad (A)$$

$$\omega_2 = 2149,935 e^{j0,579} \Omega \quad (B)$$

$$z_{2L} = \frac{j\omega L R_2}{R_2 + j\omega L}$$

$$\omega_1 = 0,4472 e^{j1,107} \quad (C)$$

$$\omega_2 = 0,8944 e^{j0,588} \quad (D)$$


$$\hat{U}_{1mL} = \frac{\hat{U}_{1m} \cdot z_{1A}}{R_1 + z_{1A}} \cdot z_{2C} = 2,6905 e^{j2,012} V$$

$$\hat{U}_{2mL} = \frac{\hat{U}_{2m} \cdot z_{1B}}{R_1 + z_{1B}} \cdot z_{2D} = 1,1695 e^{-j0,296} V$$

$$u_2(t) = 0 + 2,6905 \sin(10^3 t + 2,012) + 1,1695 \sin(3 \cdot 10^3 t - 0,296) V$$

$$U_{2ef} = \sqrt{U_0^2 + \frac{U_1^2}{2} + \frac{U_2^2}{2}} = \sqrt{0^2 + \frac{2,6905^2}{2} + \frac{1,1695^2}{2}} = 2,074 V$$

1B3H

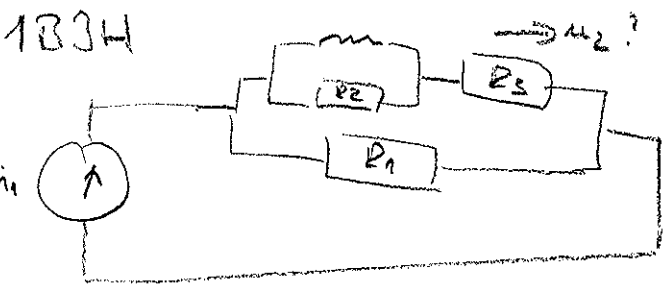

$R_1 = 2 \cdot 10^3 \Omega$ $I_0 = 1 \mu A$
 $R_2 = 2 \cdot 10^3 \Omega$ $I_1 = 10 \mu A$
 $R_3 = 4 \cdot 10^3 \Omega$ $I_3 = 2 \mu A$
 $\omega_0 = 10^3 \text{ s}^{-1}$ $\varphi_1 = \frac{\pi}{4}$ $\varphi_2 = -\frac{\pi}{3}$

$$i(t) = 1 \cdot 10^{-3} + 10^{-2} \sin\left(10^3 t + \frac{\pi}{4}\right) + 2 \cdot 10^{-3} \sin\left(3 \cdot 10^3 t + \frac{\pi}{3}\right)$$

$I_{0R_3} = \frac{I_0 \cdot R_1}{R_1 + R_3} = \frac{1 \cdot 10^{-3} \cdot 2 \cdot 10^3}{2 \cdot 10^3 + 4 \cdot 10^3} = \frac{2}{6} \cdot 10^{-3} = \frac{1}{3} \cdot 10^{-3} \text{ A}$
 $U_{R_3} = R_3 \cdot I_{0R_3} = 4 \cdot 10^3 \cdot \frac{1}{3} \cdot 10^{-3} = \frac{4}{3} \text{ V} \approx 1.33 \text{ V}$
 (Zdecij I, ta E je L zdat) $\rightarrow R_2$ ne + datu

$Z_P = \frac{R_2 \cdot j\omega L}{R_2 + j\omega L} = \frac{2 \cdot 10^3 \cdot j \cdot \omega \cdot 1}{2 \cdot 10^3 + j \cdot \omega \cdot 1}$
 $\omega_0 = 894,427 e^{j1,107} \text{ rad/s}$
 $\omega_1 = 1664,100 e^{j0,588} \text{ rad/s}$

$\hat{I}_{1R_3} = \frac{\hat{I}_{1m} \cdot R_1}{Z_P + R_1 + R_3} = \frac{10 e^{j\frac{\pi}{4}} \cdot 10^3}{2,1A + 2 \cdot 10^3 + 4 \cdot 10^3} = 1,8318 \cdot 10^{-3} e^{j0,6383} \text{ A}$


$\Rightarrow \hat{U}_{1R_3} = \hat{I}_{1R_3} \cdot R_3 = 7,3274 e^{j0,6383} \text{ V}$

$\hat{I}_{3R_3} = \frac{\hat{I}_{3m} \cdot R_1}{Z_P + R_1 + R_3} = 3,1 \cdot 10^{-3} e^{-j1,190} \text{ A} \Rightarrow \hat{U}_{2m} = 1,240 e^{-j1,190} \text{ V}$

$u(t) = 4 + 7,3274 \sin\left(10^3 t + 0,6383\right) + 1,240 \sin\left(3 \cdot 10^3 t - 1,190\right) \text{ V}$

$U_{eff} = \sqrt{U_{0m}^2 + U_{1m}^2 + U_{2m}^2} = \sqrt{4^2 + \frac{7,3274^2}{2} + \frac{1,240^2}{2}} = 6,604 \text{ V}$

134A

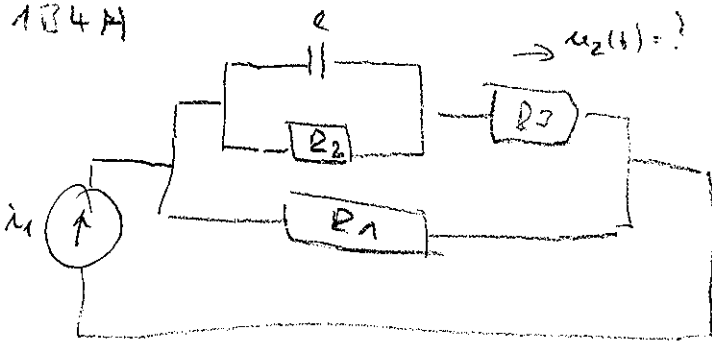

- $R_1 = 10^3 \Omega$
- $R_2 = 2 \cdot 10^3 \Omega$
- $R_3 = 4 \cdot 10^3 \Omega$
- $C = 10^{-6} F$
- $I_0 = 5 \mu A$
- $I_{m1} = 10 \mu A$
- $I_{m3} = 2 \mu A$
- $\omega = 10^3 s^{-1}$
- $\varphi_1 = \frac{\pi}{4}$
- $\varphi_2 = -\frac{\pi}{3}$

$$u(t) = I_0 + I_{m1} \sin(\omega t + \varphi) + I_{m3} \sin(3\omega t + \varphi) \rightarrow$$

$$= 5 \cdot 10^{-3} + 10^{-2} \sin(10^3 t + \frac{\pi}{4}) + 2 \cdot 10^{-3} \sin(3 \cdot 10^3 t - \frac{\pi}{3})$$

$$z_{C R_2} = \frac{R_2 \cdot C}{R_2 + C} = \frac{\frac{R_2}{j\omega C}}{R_2 + \frac{1}{j\omega C}} = \frac{R_2}{j\omega C R_2 + 1} = \frac{2 \cdot 10^3}{j \cdot 10^3 \cdot 10^{-6} \cdot 2 \cdot 10^3 + 1}$$

$$\rightarrow \omega(10^3) z_{C R_2} = 894,427 e^{-j1,107} \text{ (A)}$$

$$\rightarrow \omega(3 \cdot 10^3) z_{C R_2} = 328,797 e^{-j1,405} \text{ (B)}$$

$$\hat{I}_{0 R_3} = \frac{\hat{I}_0 \cdot R_1}{(R_1 + R_2 + R_3)} = \frac{5 \cdot 10^{-3} \cdot 10^3}{7 \cdot 10^3} = \frac{5}{1400} \rightarrow \hat{U}_{R_3} = 2,857 V$$

(c-wegpunkt n 53)

$$\hat{I}_{\varphi R_3} = \frac{\hat{I}_1 \cdot R_1}{R_1 + R_3 + z_{C R_2 A}} = \frac{10 e^{j\frac{\pi}{4}} \cdot 10^3}{5 \cdot 10^3 + 894,427 e^{-j1,107}} = 1,831 \cdot 10^{-3} e^{j0,932}$$


$$\rightarrow \hat{U}_{R_3} = 7,327 e^{j0,932} V$$

$$\hat{I}_{3 R_3} = \frac{\hat{I}_3 \cdot R_1}{R_1 + R_3 + z_{C R_2 B}} = \frac{2 \cdot 10^{-3} e^{-j\frac{\pi}{3}} \cdot 10^3}{5 \cdot 10^3 + 328,797 e^{-j1,405}} = 3,949 \cdot 10^{-4} e^{-j0,983}$$

$$\rightarrow \hat{U}_{R_3} = 1,5796 e^{-j0,983} V$$

$$u(t) = 2,857 + 7,327 \sin(10^3 t + 0,932) + 1,5796 \sin(3 \cdot 10^3 t - 0,983) V$$
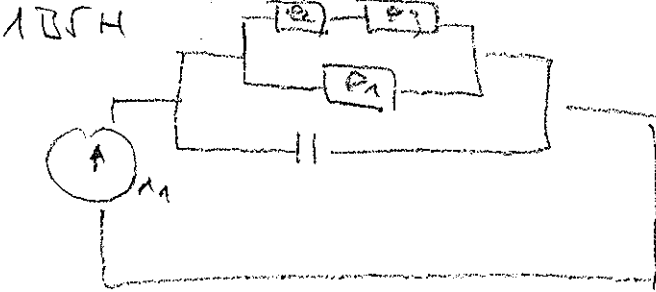
$$U_{eff} = \sqrt{\frac{U_0^2}{2} + \frac{U_1^2}{2} + \frac{U_2^2}{2}} = \sqrt{\frac{2,857^2}{2} + \frac{7,327^2}{2} + \frac{1,5796^2}{2}} = 6,021 V$$



$$R = 1, 2, 4 \cdot 10^3 \Omega$$

$$C = 10^{-6} F$$

$$\varphi = \frac{\pi}{4} ; -\frac{\pi}{4}$$

$$\omega = 10^3 \frac{1}{s}$$

$$I = 5, 10, 2 \cdot 10^{-3} A$$

$$\hat{I}_0 = \frac{\hat{I}_{0m} \cdot R_1}{R_1 + R_2 + R_3} = \frac{5 \cdot 10^{-3} \cdot 10^3}{7 \cdot 10^3} = \frac{5 \cdot 10^{-3}}{7} = \frac{1}{1400} \Rightarrow$$

$$\Rightarrow \hat{U}_0 = \frac{20}{7} = 2,857 V$$

$$\hat{I}_1 = \hat{I}_n \cdot \frac{1}{j\omega C} \cdot \frac{R_1}{\frac{1}{j\omega C} + \frac{R_1(R_2+R_3)}{R_1+R_2+R_3}} = \frac{10 e^{-j\frac{\pi}{4}} \cdot 1}{j \cdot 10^3 \cdot 10^{-6} + \frac{1 \cdot 10^3 \cdot 10^3}{7}} \cdot \frac{1}{7} =$$


$$= 1,084 \cdot 10^{-3} e^{j0,0767} \Rightarrow \hat{U}_1 = 4,3386 e^{j0,0767} V$$

$$\hat{I}_2 = \frac{1}{j\omega C} \cdot \frac{1}{\frac{1}{j\omega C} + \frac{R_1(R_2+R_3)}{R_1+R_2+R_3}} = \frac{2 \cdot 10^{-3} e^{-j\frac{\pi}{4}}}{j \cdot 3 \cdot 10^3 \cdot 10^{-6} + \frac{1 \cdot 10^3 \cdot 10^3}{7}} \cdot \frac{1}{7} =$$

$$= 1,035 \cdot 10^{-4} e^{-j2,247} \Rightarrow \hat{U}_3 = 0,4142 e^{-j2,247} V$$

$$u_2(t) = 2,857 + 4,3386 \sin(10^3 t + 0,0767) + 0,4142 \sin(3 \cdot 10^3 t - 2,247) V$$
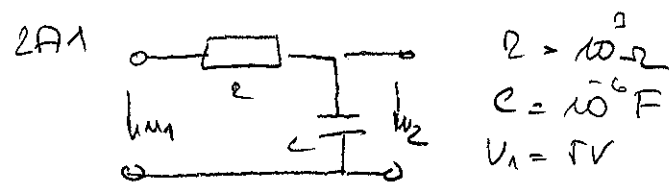
$$V_{2EFF} = \sqrt{U_0^2 + \frac{U_1^2}{2} + \frac{U_3^2}{2}} = \sqrt{2,857^2 + \frac{4,3386^2}{2} + \frac{0,4142^2}{2}} = 4,202 V$$





$$P = \frac{1}{pR} \cdot \frac{1}{R + \frac{1}{pC}} = \frac{1}{pR} \cdot \frac{pC}{1 + pCR} = \frac{1}{1 + pCR} = \frac{1}{pC} \cdot \frac{1}{p + \frac{1}{cR}} = 10^3 \cdot \frac{1}{p + 10^3}$$

$$a(p) = \frac{P(p)}{p} = \frac{10^3}{p} \cdot \frac{1}{p + 10^3} \quad \left[A = \frac{10^3}{p + 10^3} \Big|_{p=0} = 1 \right]$$

$$a(p) = \left(\frac{1}{p} - \frac{1}{p + 10^3} \right) \cdot U_1 \quad \left[B = \frac{10^3}{p} \Big|_{p=-10^3} = -1 \right]$$

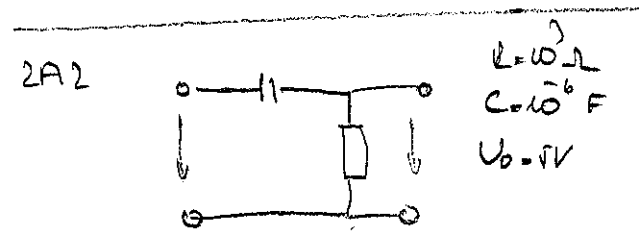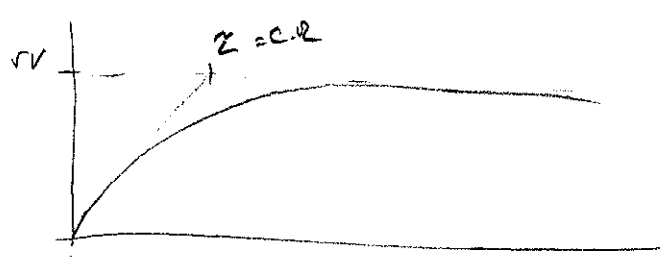
$$a(t) = 5 \cdot \left(1 - e^{-10^3 t} \right) = \underbrace{5 - 5e^{-10^3 t}}_V$$




$$P = \frac{R}{\frac{1}{pC} + R} \cdot \frac{pCR}{1 + pCR} = 1 \cdot \frac{p}{p + \frac{1}{CR}}$$

$$a(p) = \frac{U_0 \cdot P(p)}{p} = \frac{5}{p \cdot \left(p + \frac{1}{CR} \right)} = 5 \cdot \frac{1}{p + \frac{1}{CR}} = 5 \cdot e^{-\frac{1}{CR} t} = \underbrace{5e^{-10^3 t}}_V$$

$z = cR = 10^{-3}$

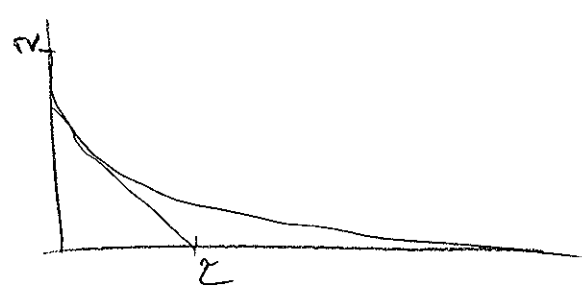

2A3

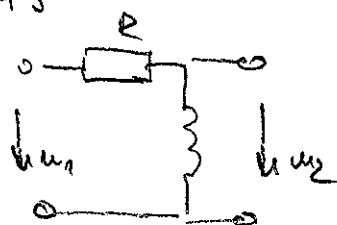


$R = 10^3 \Omega$
 $L = 1H$
 $U_1 = rV$


$$P = \frac{pL}{R+pL} = \frac{L}{L} \cdot \frac{P}{P+\frac{R}{L}} = \frac{P}{P+2}$$

$$a(t) = \frac{P(p)}{P} = \frac{1}{P+2} = \frac{10^3}{P+10^3}$$

$$a(t) = \sqrt{e^{-10^3 t}} \text{ V}$$

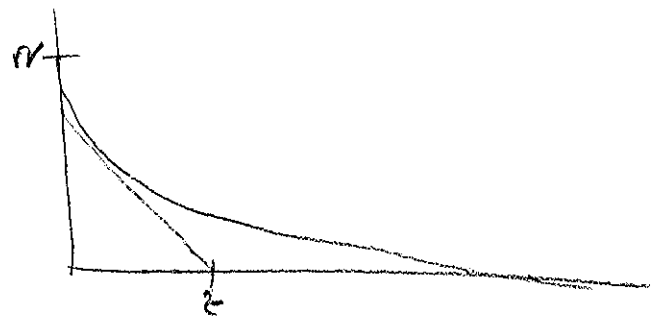

2A4

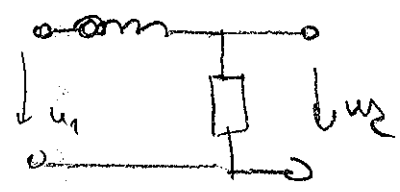

$R = 10^3 \Omega$
 $L = 1H$
 $U_1 = rV$

$$P = \frac{R}{pL+R} = \frac{R}{L} \cdot \frac{1}{P+\frac{R}{L}} = 10^3 \cdot \frac{1}{P+10^3}$$


$$a(t) = \frac{10^3}{P} \cdot \frac{1}{P+10^3} = \frac{A}{P} + \frac{B}{P+10^3}$$


$$A = \frac{10^3}{P+10^3} \Big|_{P=0} = 1$$

$$B = \frac{10^3}{P} \Big|_{P=10^3} = -1$$

$$a(t) = U_1 \left(\frac{1}{P} - \frac{1}{P+10^3} \right) \text{ V}$$
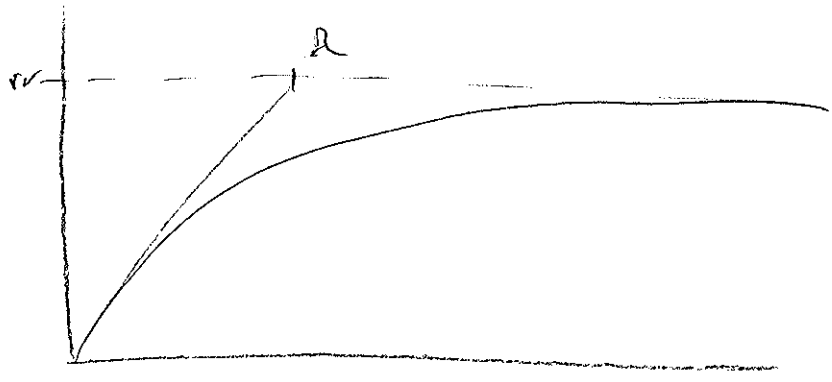
$$= \sqrt{e^{-10^3 t}} = \sqrt{1 - e^{-10^3 t}} \text{ V}$$



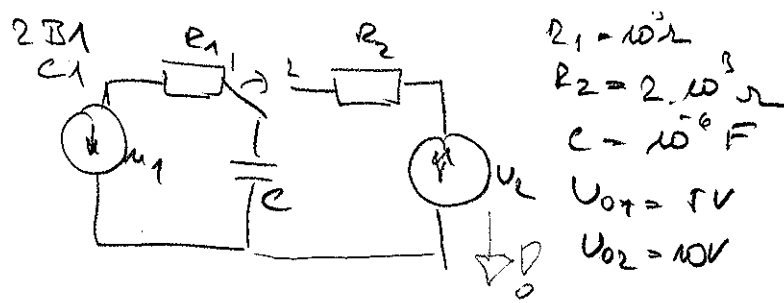

$$i = C \cdot \frac{du}{dt}$$

$$u(0^-) = 5V$$

$$u(\infty) = -10V$$

$$C \cdot \frac{du}{dt} + \frac{u_2 - u_2}{R} = 0$$

$$R \cdot C \cdot \frac{du}{dt} + u_2 + U_{02} = 0 \Rightarrow$$



$$RC\lambda + 1 = 0 \Rightarrow \lambda = \frac{-1}{RC} = -100$$

$$u(t) = k_1 \cdot e^{-100t} + u(\infty)$$


$$u(t) = k_1 \cdot e^{-100t} + (-10)$$

$$u(0) = 5 = k_1 - 10 \Rightarrow k_1 = 15$$
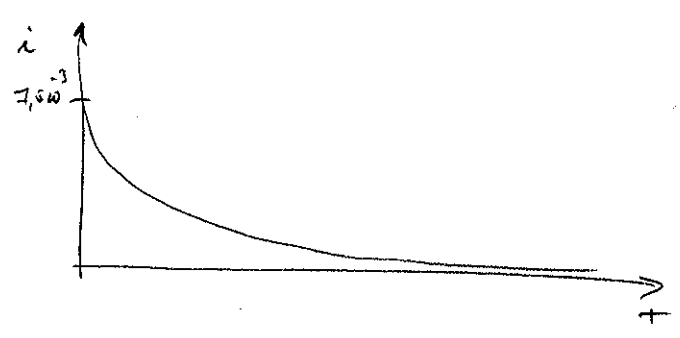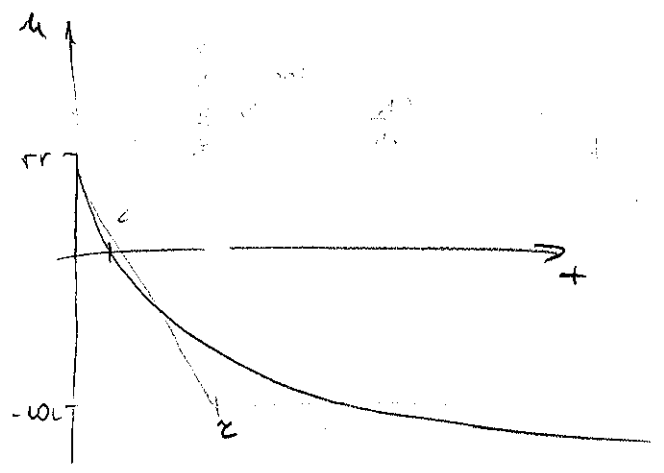
$$u(t) = 15 \cdot e^{-100t} - 10 \text{ V} \Rightarrow i = C \cdot \frac{du}{dt} = 10^{-6} \cdot (-100) \cdot 15 \cdot e^{-100t} = -7.5 \cdot 10^{-3} \cdot e^{-100t} \text{ A}$$



2 B2
C2

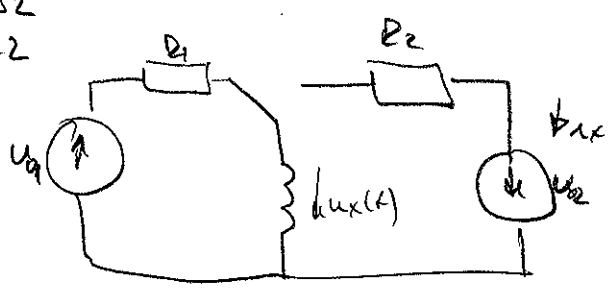

$R_1 = 10^3 \Omega$
 $R_2 = 2 \cdot 10^3 \Omega$
 $L = 1 \text{ H}$
 $U_{01} = 5 \text{ V}$
 $U_{02} = 10 \text{ V}$

$$u = L \cdot \frac{di}{dt}$$

$$i(0^-) = \frac{U_{01}}{R_1} = 0,005$$

$$i(\infty) = \frac{U_{02}}{R_2} = \frac{-10}{2 \cdot 10^3} = -0,005$$

$$L \cdot \frac{di}{dt} + R_2 \cdot i + U_{02} = 0$$

$$\frac{L}{R_2} \cdot \frac{di}{dt} + i = 0$$

$$\lambda = -\frac{R_2}{L} = -2000$$

$$i(t) = k_1 \cdot e^{-2000t} + (-0,005)$$



$$0,005 = k_1 - 0,005$$


$$k_1 = 0,01$$

$$i(t) = 0,01 \cdot e^{-2000t} - 0,005$$

$$u = L \cdot \frac{di}{dt} \Rightarrow u(t) = 1 \cdot (-2000) \cdot 0,01 \cdot e^{-2000t} =$$
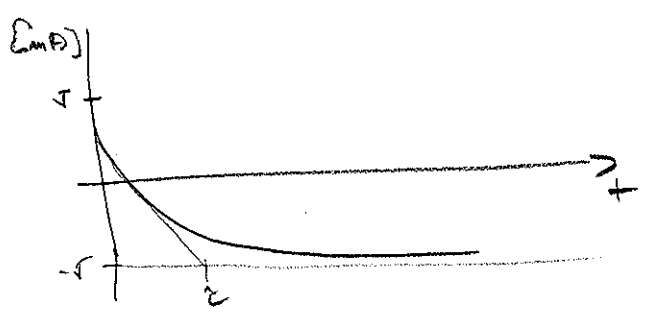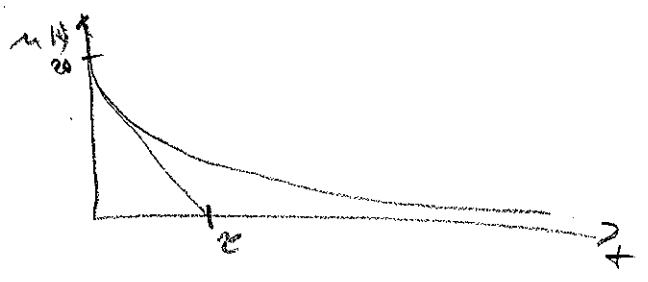
$$-20 \cdot e^{-2000t} \text{ (obtienne)}$$



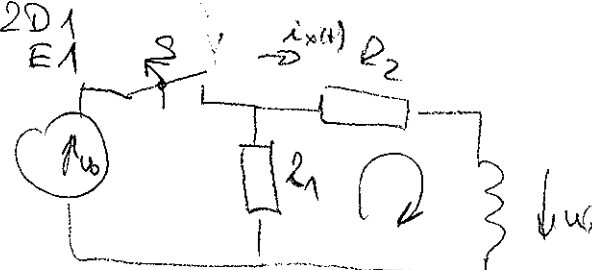

$$R_1 = 10^3 \Omega$$

$$R_2 = 2 \cdot 10^3 \Omega$$

$$L = 1H$$

$$U_0 = 10V$$

$$u = L \cdot \frac{di}{dt}$$

$$u = e \cdot I \Rightarrow I = \frac{u}{e}$$

$$i(0^-) = \frac{U_0}{R_2} = \frac{10}{2 \cdot 10^3} = 5 \cdot 10^{-3} A$$

$$i(\infty) = 0 A$$

$$L \cdot \frac{di}{dt} + R_1 \cdot i + R_2 \cdot i = 0$$

$$\tau = \frac{L}{R_1 + R_2} = \frac{1}{3 \cdot 10^3} = 3 \cdot 10^{-4} s$$

$$L \cdot \frac{di}{dt} + i \cdot (R_1 + R_2) = 0$$

$$\tau \cdot \lambda + 1 = 0$$

$$\lambda = \frac{-1}{\tau} = -\frac{1}{3 \cdot 10^{-4}} = -3 \cdot 10^3$$



$$i(t) = e^{-\lambda t} + i(\infty)$$

$$i(t) = \frac{1}{2} e^{-3000t} + 0$$


$$i(0) = 5 \cdot 10^{-3} = \frac{1}{2} \cdot 1 \Rightarrow \frac{1}{2} = 5 \cdot 10^{-3}$$

$$i(t) = 5 \cdot 10^{-3} \cdot e^{-3000t} A$$
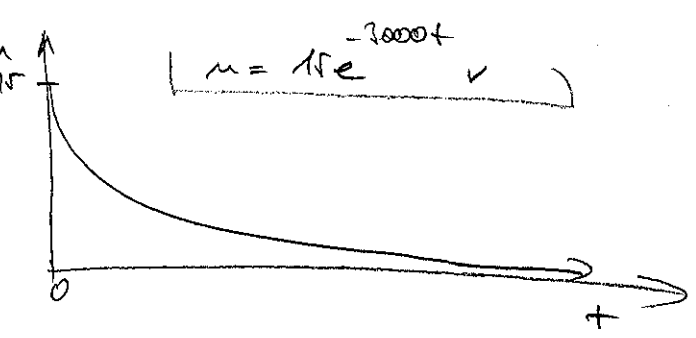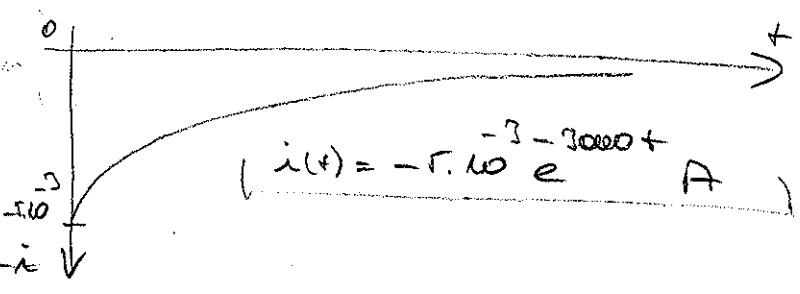
$$u = L \cdot \frac{di}{dt} = 1 \cdot (-15) \cdot e^{-3000t} = -15 \cdot e^{-3000t} V$$



2D2
E2

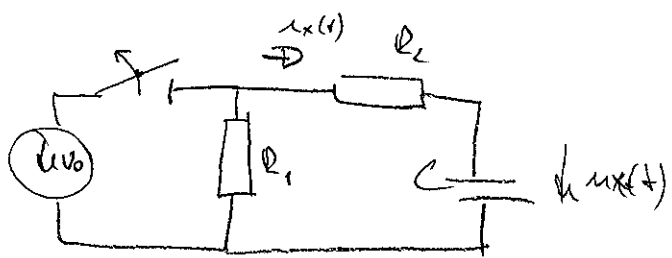

$R_1 = 10^3 \Omega$
 $R_2 = 2 \cdot 10^3 \Omega$
 $C = 10^{-6} F$
 $U_0 = 10V$

$u(0^-) = 10V$
 $u(\infty) = 0V$

$$C \cdot \frac{du}{dt} + \frac{R_1 C}{R_1} \frac{du}{dt} + \frac{U_c - U_0}{R_2} = 0$$

$$C \cdot \frac{du}{dt} + \frac{u_c}{R_1} + \frac{u_c}{R_2} - \frac{U_0}{R_2} = 0$$

? at po
ustaleno



$$C \cdot \lambda + \frac{1}{R_1} + \frac{1}{R_2} = 0 \Rightarrow \lambda = \frac{-1}{(R_1 + R_2)} \cdot \frac{1}{C} = -333,3$$

$$u_x(t) = \frac{1}{R_1} \cdot e^{-333,3t}, \quad R_1 = 10$$


$$u_x(t) = 10 e^{-333,3t} \text{ V}$$

$$i_x(t) = C \cdot \frac{du}{dt} = 10^{-6} \cdot (-333,3) \cdot e^{-333,3t} \text{ A}$$
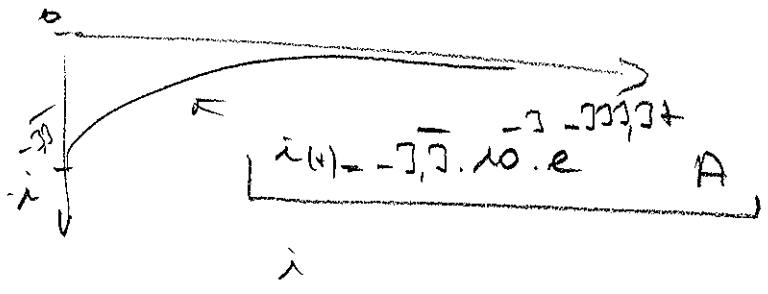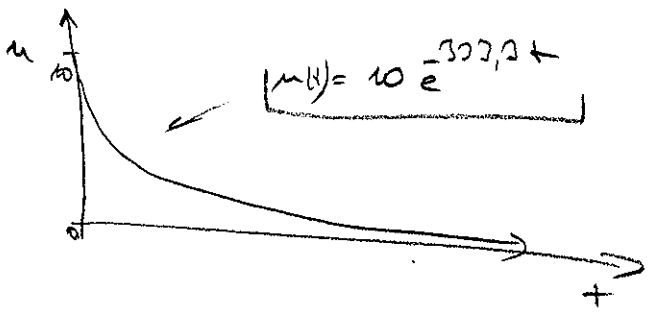
$$i_x(t) = -3,3 \cdot 10^{-3} \cdot e^{-333,3t} \text{ A}$$



2D3
E3

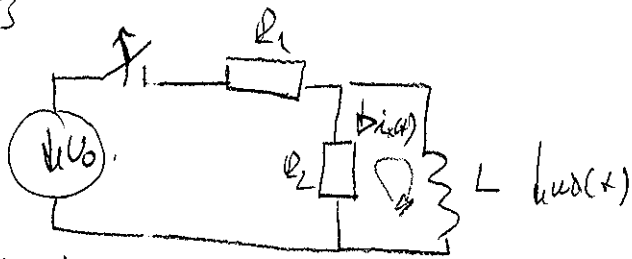

$$R_1 = 10^3 \Omega$$

$$R_2 = 2 \cdot 10^3 \Omega$$

$$L = 1 \text{ H}$$

$$U_0 = 10 \text{ V}$$

$$U = R \cdot I$$

$$i(0) = \frac{U_0}{R_1} = \frac{10}{10^3} = 0,01 \text{ A}$$

$$R_2(0) = - \frac{U_0 \cdot R_2}{R_1 + R_2} = -10$$

$$i(\infty) = 0 \text{ A}$$

$$L \frac{di}{dt} + R_2 i = 0$$

$$\lambda = - \frac{R_2}{L} = -2000$$



$$\frac{L}{R_2} \lambda + 1 = 0 \rightarrow$$

$$i_x(t) = k_1 \cdot e^{-2000t}$$


$$0,01 = k_1$$

$$i_x(t) = -0,01 e^{-2000t} \text{ A}$$
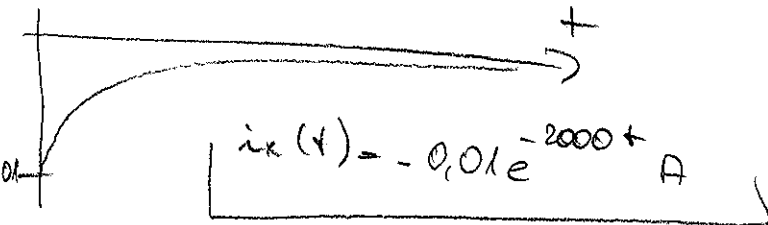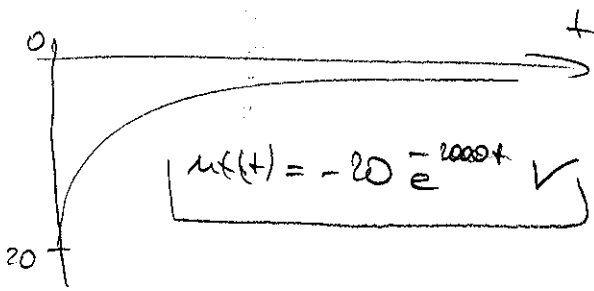
$$u = L \cdot \frac{di}{dt} = 1 \cdot (-20) \cdot e^{-2000t} = -20 \cdot e^{-2000t} \text{ V}$$



2D9
E4

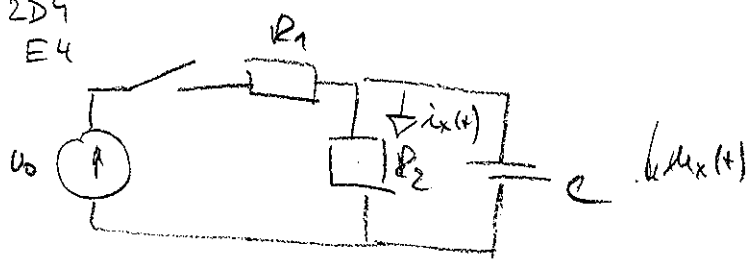

$R_1 = 10^3 \Omega$
 $R_2 = 2 \cdot 10^3 \Omega$
 $C = 10^{-6} F$
 $U_0 = 10V$

$i = C \frac{du}{dt}$

$u(0) = U_0 \cdot \frac{R_2}{R_1 + R_2} = \frac{10 \cdot 2 \cdot 10^3}{3 \cdot 10^3} = \frac{20}{3} = 6,67 V$
 $u(\infty) = 0$



$C \frac{du}{dt} + \frac{u}{R_2} = 0$

$R_2 C \cdot \lambda + 1 = 0 \Rightarrow \lambda = -\frac{1}{R_2 C} = -\frac{1}{2 \cdot 10^{-3}} = -500$


$u_x(t) = k_1 \cdot e^{-500t} + 0$

$-6,67 = k_1 \Rightarrow u_x(t) = -\frac{20}{3} e^{-500t} V$

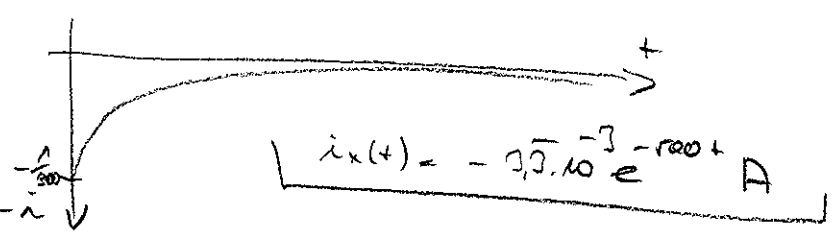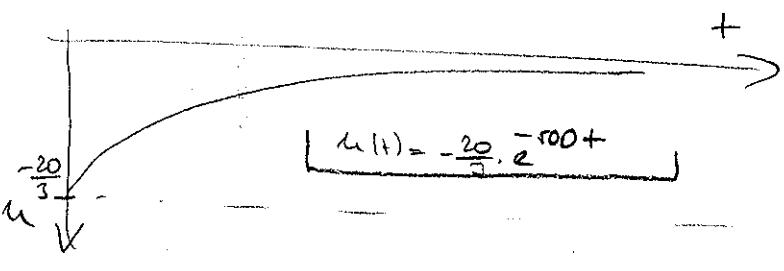$-i_x(t) = C \cdot \frac{du}{dt} = 10^{-6} \cdot \frac{-500 \cdot 20}{3} \cdot e^{-500t} = -3,3 \cdot 10^{-3} e^{-500t} A$



2FA
61

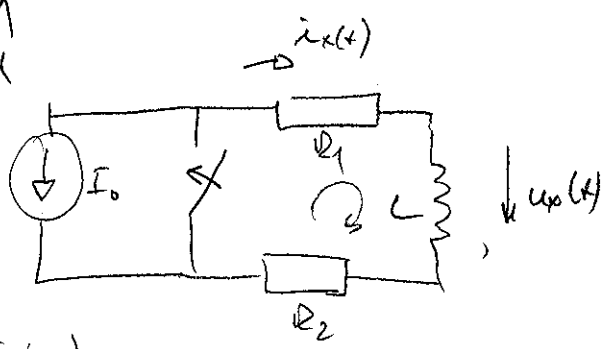

$$R_1 = 10 \Omega$$

$$R_2 = 2 \cdot 10 \Omega$$

$$L = 1 \text{ H}$$

$$I_0 = 0,01 \text{ A}$$

$$i(0_-) = -0,01 \text{ A}$$

$$i(\infty) = 0$$



$$L \cdot \frac{di}{dt} + R_1 i + R_2 i = 0$$

$$\frac{L}{R_1 + R_2} \cdot \lambda + 1 = 0 \Rightarrow \lambda = -\frac{R_1 + R_2}{L} = -3000$$


$$i_k(t) = \lambda_1 \cdot e^{-3000t} + 0$$

$$t(0) \quad -0,01 = \lambda_1 \cdot 1 \Rightarrow i_k(t) = -0,01 \cdot e^{-3000t} \text{ A}$$
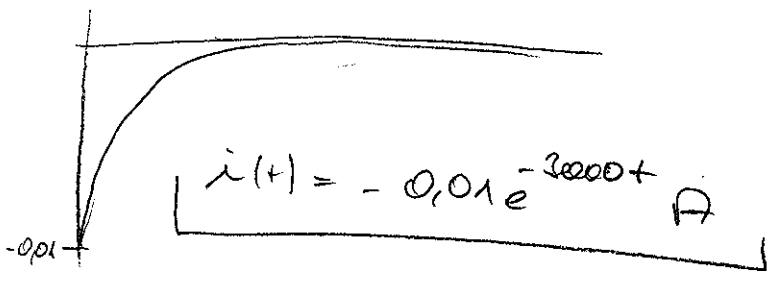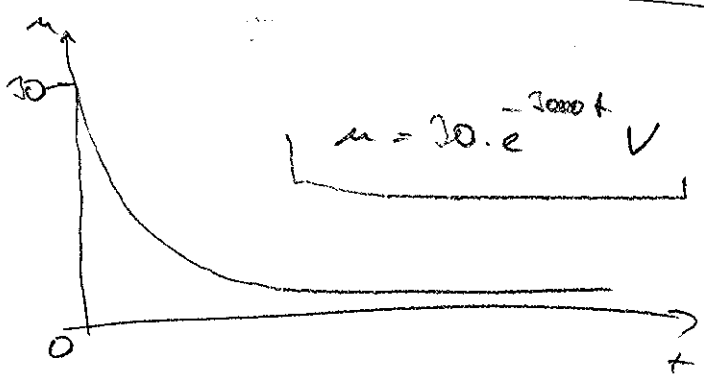
$$u = L \cdot \frac{di}{dt} = 30 \cdot e^{-3000t} \text{ V}$$



2FL
G2

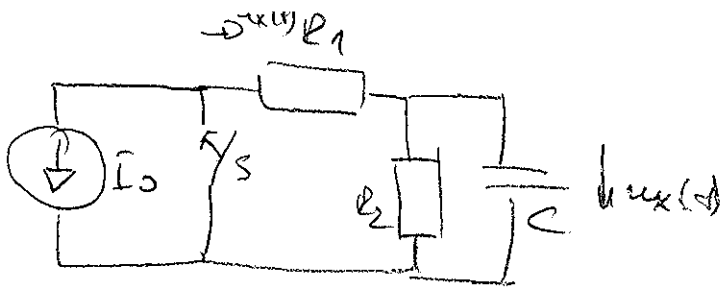

$R_1 = 10^3 \Omega$
 $R_2 = 2 \cdot 10^3 \Omega$
 $C = 10^{-6} F$
 $I_0 = 0,01 mA$

$u_C(0) = -I_0 \cdot R_2 = -20V$
 $u_C(\infty) = 0$

$R_i = \frac{R_2 \cdot R_1}{R_2 + R_1} = 666,6 \Omega$
 НАХРАТЕНИ!

$C \cdot \frac{du_C}{dt} + \frac{u_C}{R_2} = 0$

$C R_2 \cdot \lambda + 1 = 0 \Rightarrow \lambda = -1$
 $\frac{-1}{C R_2} = -1500$



$u_C(t) = \lambda_1 \cdot e^{-1500t} + 0$

$-20 = \lambda_1$


$u_C(t) = -20 \cdot e^{-1500t} V$

$i = C \cdot \frac{du_C}{dt} = 10^{-6} \cdot (-1500) e^{-1500t} = 0,0015 e^{-1500t} A$

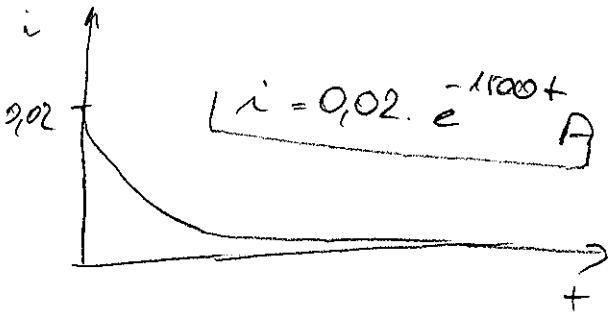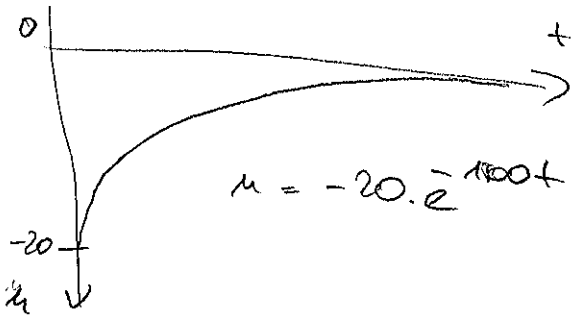покажем $I_0 = -0,01 A \Rightarrow i_K(t) = 0,02 \cdot e^{-1500t} A$



263

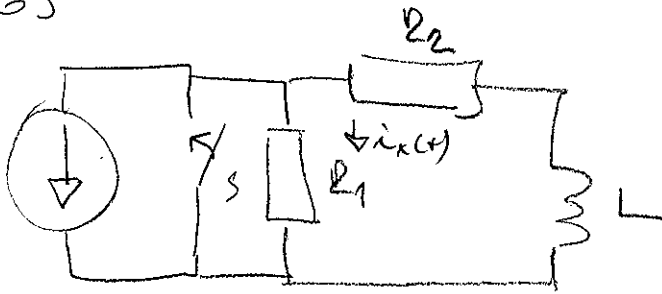

$$i(0) = 10 \text{ mA}$$

$$i(\infty) = 0$$

$$L \cdot \frac{di}{dt} + R_2 i = 0$$

$$\frac{L}{R_2} \cdot \lambda + 1 = 0 \quad \Rightarrow \quad \lambda = -\frac{R_2}{L} = -2000$$

$$i_x(t) = I_0 \cdot e^{-2000t}$$

$$i_x(t) = -0,01 \cdot e^{-2000t}$$

$$u = L \cdot \frac{di}{dt} = 20 e^{-2000t}$$

$$R_1 = 10^3 \Omega$$

$$R_2 = 2 \cdot 10^3 \Omega$$


$$L = 1 \text{ H}$$

$$I_0 = 10 \text{ mA}$$

NUTZRAFFENWERT

$$R_i = \frac{R_1 \cdot R_2}{R_1 + R_2} = 666,67 \Omega$$

4A1A

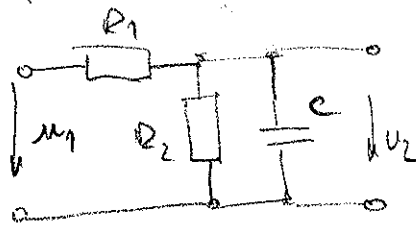

$R_1 = 10^3 \Omega$
 $R_2 = 4 \cdot 10^3 \Omega$
 $C = 10^{-6} F$

$P = \frac{U_2}{U_1}$


$$U_2 = \frac{R_2 \cdot \frac{1}{j\omega C}}{R_2 + \frac{1}{j\omega C}} = \frac{\frac{R_2}{j\omega C}}{\frac{j\omega C R_2 + 1}{j\omega C}} = \frac{R_2}{j\omega C R_2 + 1}$$

$$U_1 = \frac{R_1 + R_2}{j\omega C R_2 + 1} = \frac{j\omega C R_1 R_2 + R_1 + R_2}{j\omega C R_2 + 1}$$

$$P = \frac{U_2}{U_1} = \frac{\frac{R_2}{j\omega C R_2 + 1}}{\frac{j\omega C R_1 R_2 + R_1 + R_2}{j\omega C R_2 + 1}} = \frac{R_2}{j\omega C R_1 R_2 + R_1 + R_2}$$

$$= \frac{R_2}{C R_1 R_2} \cdot \frac{1}{j\omega + \frac{R_1 + R_2}{C R_1 R_2}} = \frac{1000}{j\omega + 1250}$$

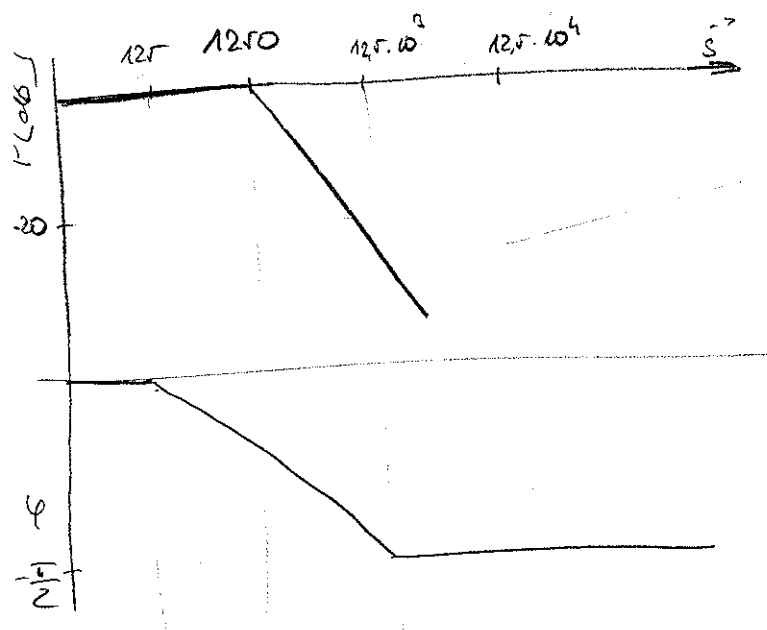$\omega = 1000 \text{ s}^{-1}$
 $k = \frac{4}{1} = 0,4$



$P = \frac{1}{\frac{\omega}{\omega_0}} = \frac{\omega_0}{\omega} \Rightarrow \text{klesat}$

4A1B

Piechodová charakteristika

$$e(t) \frac{1}{P(s)} = \frac{0,8}{s} \cdot \frac{1000}{s+1250} = \frac{1000A}{s} + \frac{B}{s+1250}$$


$$1000 = Ap + A1250 + Bp \quad ; \quad A+B=0$$

$$1250A = 1000$$

$$A = \frac{1}{1250} = 0,8$$

$$B = -0,8$$

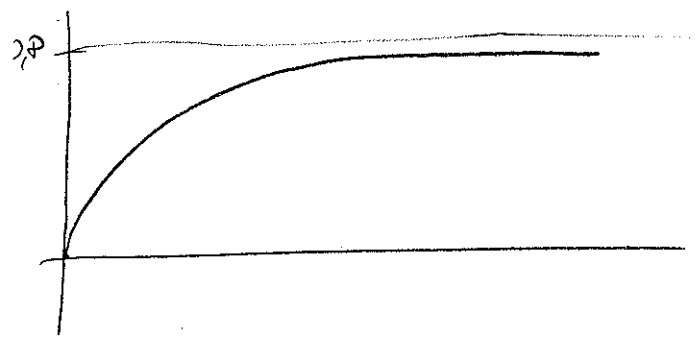
$$\frac{1000}{s(s+1250)} = \frac{0,8}{s} - \frac{0,8}{s+1250} \Rightarrow \left[0,8 - 0,8e^{-1250t} \right]$$




4A1C

Impulsová charakteristika
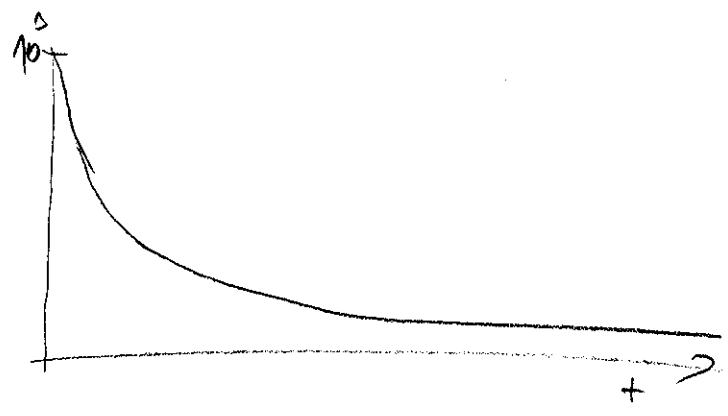
$$w(t) \frac{1000}{s+1250} \Rightarrow 1000e^{-1250t}$$



4A2A

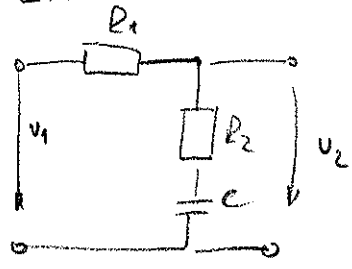


$R_1 = 4 \cdot 10^3 \Omega$
 $R_2 = 1 \cdot 10^3 \Omega$
 $C = 10^{-6} F$

$u_2 = R_2 + \frac{1}{j\omega C} = \frac{j\omega C R_2 + 1}{j\omega C}$
 $u_1 = \frac{j\omega C \cdot (R_1 + R_2) + 1}{j\omega C}$

$$P = \frac{u_2}{u_1} = \frac{j\omega C R_2 + 1}{j\omega C (R_1 + R_2) + 1} = \frac{C R_2}{C (R_1 + R_2)} \cdot \frac{P + \frac{1}{C R_2}}{P + \frac{1}{C (R_1 + R_2)}} = \frac{1}{r} \cdot \frac{P + 1000}{P + 200}$$

$\omega_1 = 1000 \text{ s}^{-1} \nearrow$
 $\omega_2 = 200 \text{ s}^{-1} \searrow$

$\omega_2 < \omega_1$

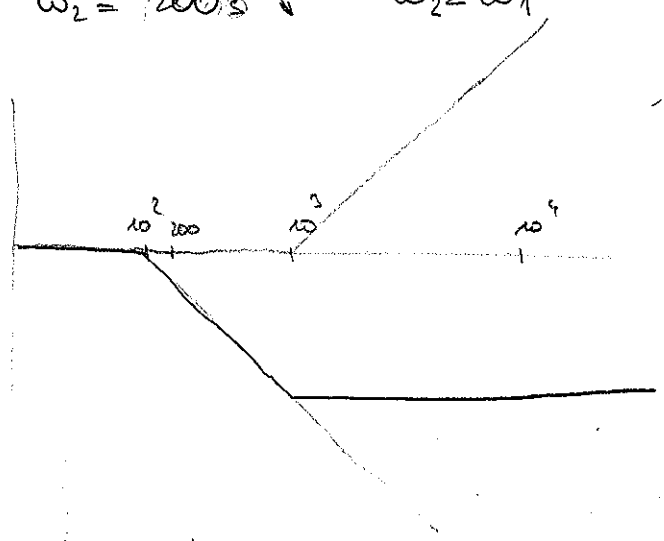


$a(f) = \frac{P(\omega)}{P} = \frac{0,2}{P} \cdot \frac{P + 1000}{P + 200} = \frac{A}{P} + \frac{B}{P + 200} = \frac{1}{P} - \frac{0,8}{P + 200} \Rightarrow$

$0,2P + 200 = A(P + 200) + B P$

$0,2P = A + B \Rightarrow B = -0,8$


$200 = 200A \Rightarrow A = 1$

$\Rightarrow 1 - 0,8 e^{-200/\omega}$

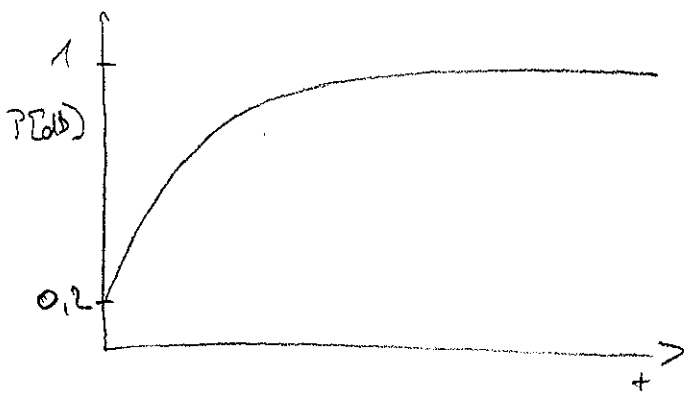


4A2B
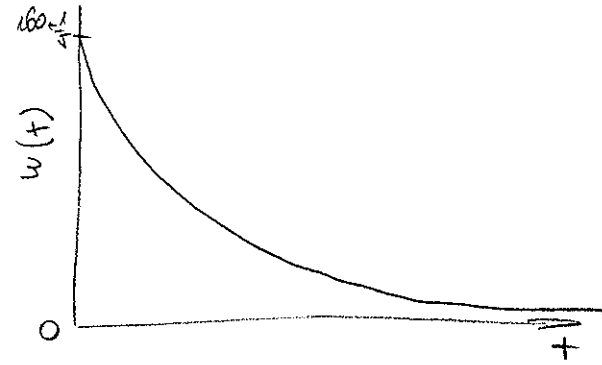
$$P = \frac{1}{s} \cdot \frac{p+1000}{p+200} = \frac{1}{s} \cdot \left(\frac{p+200+800}{p+200} \right) = \frac{1}{s} \cdot \left(1 + \frac{800}{p+200} \right)$$
$$= \frac{1}{s} + 160 e^{-200t} = w(t)$$



4A4A

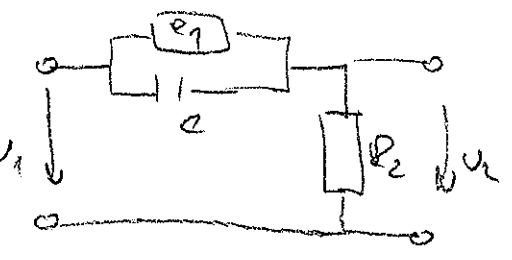

$$u_2 = R_2 \cdot \frac{1}{R_1 + \frac{1}{j\omega C}} + R_2 = \frac{R_1}{j\omega C R_1} + R_2 =$$

$$= \frac{j\omega C R_1 R_2 + R_1}{j\omega C R_1}$$

$$P = \frac{u_2}{u_1} = \frac{R_2 \cdot j\omega C R_1}{j\omega C R_1 R_2 + R_1} = \frac{j\omega C R_1 R_2}{j\omega C R_1 R_2 + R_1} = \frac{C R_1 R_2}{C R_1 R_2} \cdot \frac{P}{P + \frac{R_1}{C R_1 R_2}}$$

$$= \frac{P}{P + \frac{1}{C R_2}} = \frac{P}{P + 1000}$$

$$\frac{R_2}{R_1 + R_2} \cdot \frac{1 + j\frac{\omega}{\omega_0}}{1 + j\frac{\omega}{\omega_1}}$$

$$P = \frac{R_2}{R_2 + \frac{R_1/pC_1}{R_1 + pC_1}}$$

$$= \frac{R_2}{R_2 + \frac{R_1}{pC_1 R_1 + 1}}$$

$$= \frac{pC_1 R_1 R_2 + R_2}{pC_1 R_1 R_2 + R_2 + R_1}$$

$$= \frac{P + 250}{P + 1250} \Rightarrow k=1$$

$$R_2 + \frac{R_1}{pC_1 R_1 + 1} = \frac{R_2 (pC_1 R_1 + 1) + R_1}{pC_1 R_1 + 1}$$

$$= \frac{R_2 \cdot (pC_1 R_1 + 1) + R_1}{pC_1 R_1 R_2 + R_2 + R_1}$$

$$= \frac{C R_1 R_2}{C R_1 R_2} \cdot \frac{P + \frac{1}{C_1 R_1}}{P + \frac{R_2 + R_1}{C R_1 R_2}}$$

$\omega_1 = 250$
 $\omega_2 = 1250$

4AT

$$P = \frac{\frac{R_1}{pC_2}}{R_1 + \frac{1}{pC_2}} = \frac{R_1}{pC_2R_1 + 1} = \frac{R_1}{pC_2R_1 + 1} = \frac{R_1}{pC_2R_1 + 1 + pC_1R_1} = \frac{R_1}{pC_1(pC_2R_1 + 1)}$$

$$\frac{1}{pC_1} + \frac{R_1}{pC_2} = \frac{1}{pC_1} + \frac{R_1}{pC_2R_1 + 1} = \frac{pC_2R_1 + 1 + pC_1R_1}{pC_1(pC_2R_1 + 1)}$$

$$\frac{pC_1R_1}{p(R_1(C_1+C_2)) + 1} = \frac{C_1R_1}{R_1(C_1+C_2)} \cdot \frac{p}{p + \frac{1}{R_1(C_1+C_2)}} = \frac{4}{\sqrt{p+200}} \cdot \frac{p}{p+200}$$

$$z = 20 \log(0, P) = -2$$

$$w(t) = 0, P \left(\frac{p+200 - 200}{p+200} \right) = 0, P \left(1 - \frac{200}{p+200} \right) = \left[0, P - 160 e^{-200t} \right]$$

$$a(t) = \frac{0, P}{p} \cdot \frac{p}{p+200} = \frac{4}{\sqrt{p+200}} = \left[0, P e^{-200t} \right]$$

$$A = \frac{0, P p}{p+200} \Big|_{p=0} = 0$$

$$B = \frac{0, P p}{p} \Big|_{p=-200} = \frac{-160}{-200} = \frac{4}{\sqrt{p}}$$

1AF

$$P = \frac{\frac{1}{pC_2} + R_1}{\frac{1}{pC_1} + \frac{1}{pC_2} + R_1} = \frac{\frac{pC_2R_1 + 1}{pC_2}}{\frac{pC_2 + pC_1 + pC_1pC_2R_1}{pC_1 \cdot pC_2}} = \frac{pC_1 \cdot pC_2R_1 + pC_1}{pC_1 \cdot pC_2R_1 + pC_2 + pC_1} = \frac{p(pC_1 \cdot C_2 \cdot R_1 + C_1)}{p(pC_1 \cdot C_2 \cdot R_1 + C_2 + C_1)}$$

$$= \frac{C_1 \cdot C_2 \cdot R_1}{C_1 \cdot C_2 \cdot R_1} \cdot \frac{p + \frac{1}{C_2R_1}}{p + \frac{C_2 + C_1}{C_1C_2R_1}} = 1 \cdot \frac{p + 250}{p + 1250}$$

$$w(t) = 1 - \frac{1000}{p+1250} = \left[1 - 1000 e^{-1250t} \right]$$

$$a(t) = \frac{p+250}{p(p+1250)} = \left[0, 2 - 0, P e^{-1250t} \right]$$

$$A = \frac{p+250}{p+1250} \Big|_{p=0} = \frac{1}{\sqrt{p}}$$

$$B = \frac{p+250}{p} \Big|_{p=-1250} = \frac{4}{5}$$

487

$$\gamma = \frac{pL_2}{p(L_1+L_2) + R_1} = \frac{L_2}{L_1+L_2} \cdot \frac{p}{p + \frac{R_1}{L_1+L_2}} = \frac{4}{5} \cdot \frac{p}{p+200}$$

$$\xi = 20 \cdot \log(0,8) = -2$$

$$w(t) = 0,8 \cdot \left(1 - \frac{200}{p+200}\right) = \left[0,8 - 160 \cdot e^{-\frac{200}{p}t}\right]$$


488

$$\begin{aligned} P &= \frac{pL_2}{pL_2 + \frac{R_1 \cdot pL_1}{R_1 + pL_1}} = \frac{pL_1 \cdot pL_2 + pL_2 \cdot R_1}{pL_1 \cdot R_1 + pL_1 pL_2 + pL_2 R_1} = \frac{p \cdot (pL_1 \cdot L_2 + R_1 \cdot L_2)}{p \cdot (pL_1 \cdot L_2 + R_1 \cdot (L_1 + L_2))} = \\ &= \frac{L_1 \cdot L_2}{L_1 \cdot L_2} \cdot \frac{p + \frac{R_1}{L_1}}{p + \frac{R_1 \cdot (L_1 + L_2)}{L_1 \cdot L_2}} = \frac{p + 250}{p + 1250} \end{aligned}$$

$$w(t) = 1 - 1000 e^{-\frac{1250}{p}t}$$

$$a(t) = 0,2 + 0,8 e^{-\frac{1250}{p}t}$$

4AP

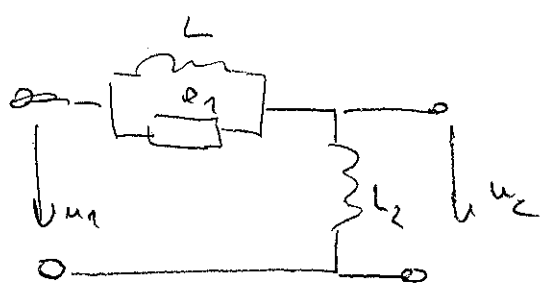


$$P = \frac{pL_2}{pL_2 + \frac{pL_1 R_1}{pL_1 + R_1}} = \frac{pL_2}{\frac{pL_2(pL_1 + R_1) + pL_1 R_1}{pL_1 + R_1}} = \frac{p(pL_1 + R_1) \cdot L_2}{p(L_2(pL_1 + R_1) + L_1 R_1)}$$

$$= \frac{pL_1 L_2 + R_1 L_2}{pL_1 L_2 + R_1 L_2 + L_1 R_1} = \frac{L_1 L_2}{L_1 L_2} \cdot \frac{p + \frac{R_1 L_2}{L_1}}{p + \frac{R_1(L_1 + L_2)}{L_1 L_2}}$$

$$\frac{p + 250}{p + 1250}$$
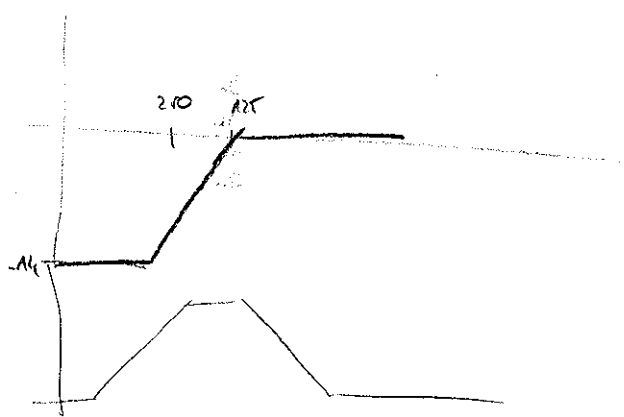
$$20 \log \left(\frac{250}{1250} \right) = -14$$



$$w(t) = \frac{p + 1250 - 1000}{p + 1250} = 1 - 1000 e^{-1250t}$$

$$a(t) = \frac{p + 250}{p(p + 1250)} = \frac{A}{p} + \frac{B}{p + 1250} \quad ; \quad A = \frac{p + 250}{p(p + 1250)} \Big|_{p=0} = \frac{250}{1250} = \frac{1}{5}$$

$$B = \frac{p + 250}{p(p + 1250)} \Big|_{p=-1250} = \frac{-4}{-1250} = \frac{4}{1250}$$

$$a(t) = \left[0.2p - 0.1p e^{-1250t} \right] \Rightarrow \text{graf}$$

4A8

$$P = \frac{\frac{1}{pC_2}}{\frac{1}{pC_2} + \frac{R_1}{pL_1}} = \frac{\frac{1}{pC_2}}{\frac{1}{pC_2} + \frac{R_1}{pC_1R_1+1}} = \frac{\frac{1}{pC_2}}{\frac{pC_1R_1+1 + pC_2R_1}{(pC_1R_1+1)pC_2}} = \frac{pC_1R_1+1}{p(R_1(C_1+C_2))+1}$$

$$= \frac{C_1 \cdot R_1}{R_1 \cdot (C_1+C_2)} \cdot \frac{p + \frac{1}{C_1 \cdot R_1}}{p + \frac{1}{R_1 \cdot (C_1+C_2)}} = \frac{1}{\sqrt{}} \cdot \frac{p + 1000}{p + 200}$$

$$\lambda = 20 \cdot \log(0,2) = -14$$

$$w(t) = 0,2 \cdot \left(1 + \frac{800}{p+200} \right) = \left(0,2 + 160e^{-200t} \right)$$

$$a(t) = \frac{0,2p+200}{p \cdot (p+200)} = \frac{1 - 0,2p}{p(p+200)}$$

$$= \left(1 - 0,2e^{-200t} \right)$$

$$A = \frac{0,2p+200}{p+200} \Big|_{p=0} = 1$$

$$B = \frac{0,2p+200}{p} \Big|_{p=-200} = \frac{160}{-200} = -\frac{4}{5}$$

4B2

$$P = \frac{pL_1+R_2}{pL_1+R_1+R_2} = \frac{L_1}{L_1} \cdot \frac{p + \frac{R_2}{L_1}}{p + \frac{R_1+R_2}{L_1}} = 1 \cdot \frac{p + 1250}{p + 1250} = \left(\frac{p + 1250}{p + 1250} \right) ?$$

$$w(t) = 1 - \frac{1000}{p+1250} = \left(1 - 1000e^{-1250t} \right)$$

$$a(t) = \frac{p+250}{p \cdot (p+1250)} = \left(0,2 + 0,2e^{-1250t} \right)$$

$$A = \frac{p+250}{p+1250} \Big|_{p=0} = \frac{1}{5}$$

$$B = \frac{p+250}{p} \Big|_{p=-1250} = \frac{-1000}{-1250} = \frac{4}{5}$$

1.1

$L = 0,5 \cdot 10^{-6} \text{ H} \cdot \text{m}^{-1}$
 $C = 10 \cdot 10^{-12} \text{ F} \cdot \text{m}^{-1}$
 $t_0 = 0,05 \cdot 10^{-6} \text{ s}$
 $U_a = \frac{U_0}{2} \cdot \varphi$

$s = \pi \cdot t \Rightarrow s = \frac{1}{\sqrt{L \cdot C}} \cdot t = \frac{1}{\sqrt{0,5 \cdot 10^{-6} \cdot 10 \cdot 10^{-12}}} \cdot 0,05 \cdot 10^{-6}$
 $= 10 \text{ m} \quad (\text{pro } U_a = U_0) \cdot \varphi \Rightarrow$
 $s = 5 \text{ m} \quad (\text{pro } U_a = \frac{U_0}{2})$

1.2

$R_s = R_0$
 $L = \dots$
 $C = \dots$




$R_0 = \sqrt{\frac{L}{C}} = \sqrt{\frac{0,5 \cdot 10^{-6}}{10 \cdot 10^{-12}}} = 100 \Omega$

1.3

$L_i C_i = \dots$
 $U_i = 50 \text{ V}$
 $l = 100 \mu\text{m}$
 $t_0 = 0,01 \cdot 10^{-6} \text{ s}$

$U_p = U_i \cdot \frac{R_0}{R_i + R_0} = U_i \cdot \frac{R_0}{2R_0} = \frac{U_i}{2} = 5 \text{ V}$
 $s = \pi \cdot t \Rightarrow t_c = \frac{l}{v} = l \cdot \sqrt{L \cdot C} = 0,5 \cdot 10^{-6} \text{ s}$
 (doba limitu než doletí na konec)

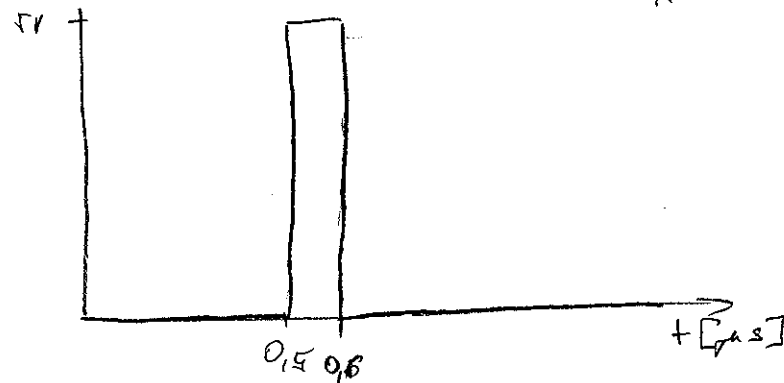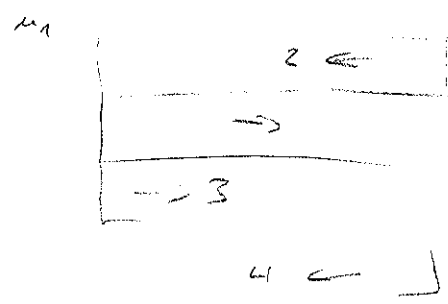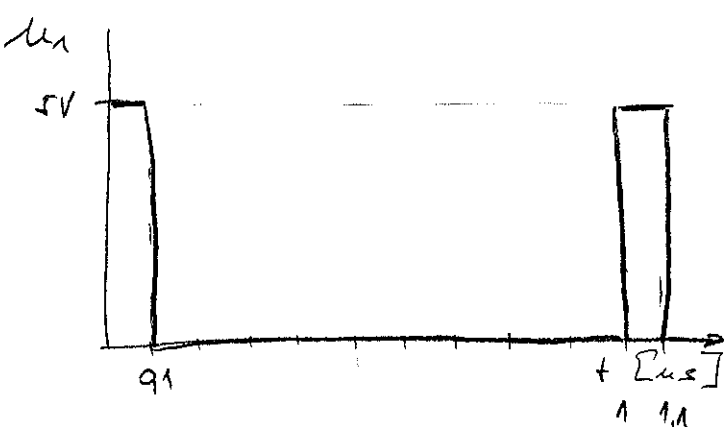
$R_s = 0 \Rightarrow \begin{cases} U_{\text{konec}} = U_{\text{start}} \\ I_{\text{konec}} = 0 \end{cases}$
 $R_i \neq R_0 \Rightarrow \varphi = 1$



T.4
 $L = 0,1 \cdot 10^{-6} \text{ H}$
 $C = 50 \cdot 10^{-12} \text{ F}$



$U_i = 10 \text{ V}$
 $l = 100 \text{ m}$
 $t = 0,1 \cdot 10^{-6} \text{ s}$

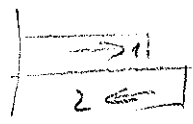$R_i = R_0$
 $R_s = \infty \Rightarrow \rho = -1 = u_2 = 0$



$$U_p = U_i \cdot \frac{R_0}{2R_0} = 5 \text{ V}$$
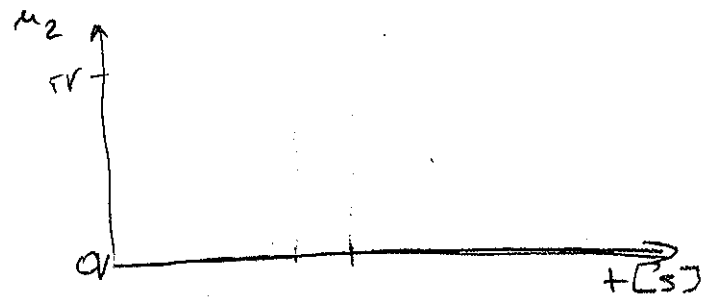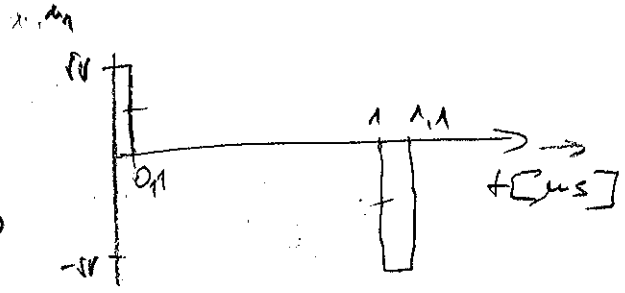
$$t_c = \frac{l}{v} = l \sqrt{LC} = 0,1 \cdot 10^{-6} \text{ s}$$




T.5
 $U_i, U_p, R_i, t = -l$

$R_s = R_0 \Rightarrow \rho = 0$

$$U_p = 5 \text{ V}$$

$$t_c = 0,1 \cdot 10^{-6} \text{ s}$$


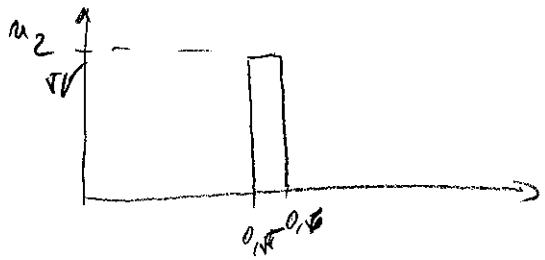


5.6
 $U_i = U_i$, $R_i = R_0$
 $R_s = 3R_0$
 $R_i = R_0$

$$U_p = U_i \cdot \frac{R_0}{R_i + R_0} = 5V$$

$$U_z = U_p \cdot \beta = U_p \cdot \frac{R_s - R_0}{R_s + R_0} = 5 \cdot \frac{(3-1) \cdot R_0}{(3+1) \cdot R_0} = 2,5V$$



$t = 0,5 \cdot 10^{-6} s$

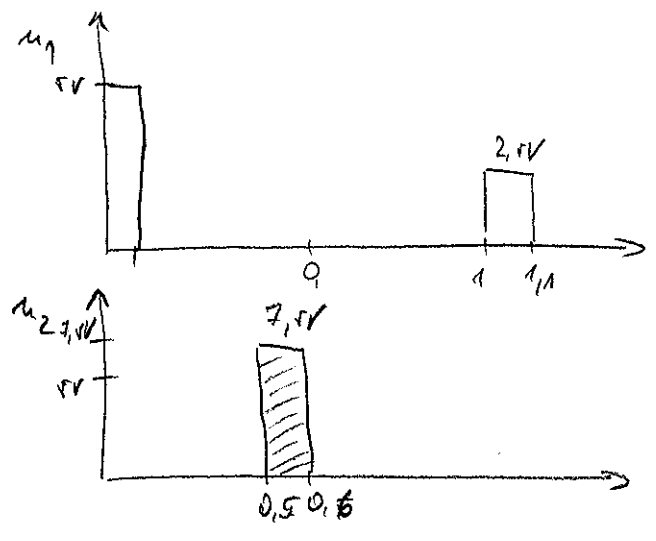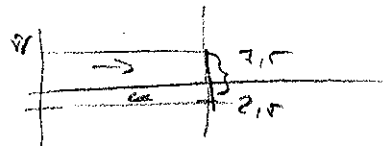

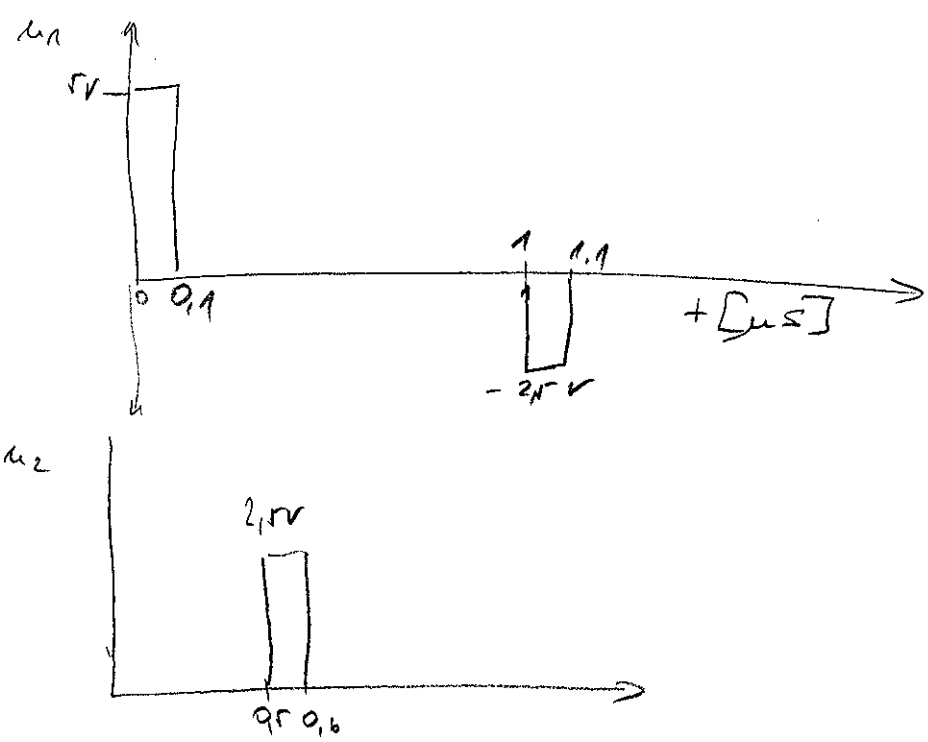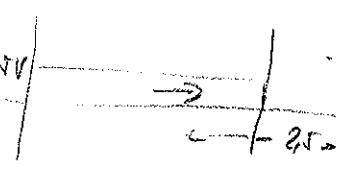
5.7.
 $R_s = \frac{1}{3} R_0$
 $R_i = R_0$

$$U_p = U_i \cdot \frac{R_0}{R_i + R_0} = U_i \cdot \frac{1}{2} = 5V$$

$$U_z = U_p \cdot \beta = U_p \cdot \frac{R_s - R_0}{R_s + R_0} = 5 \cdot \frac{(\frac{1}{3} - \frac{2}{3}) \cdot R_0}{(\frac{1}{3} + \frac{2}{3}) \cdot R_0} = 5 \cdot \frac{-\frac{2}{3}}{\frac{4}{3}} = -2,5V$$



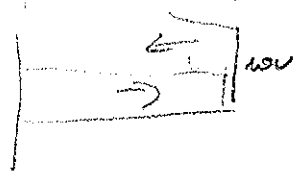r.p.
 $L, C, U_{i0} = 10V, l = 100\mu m$
 $R_i = R_0$
 $R_s = \infty \Rightarrow \beta = 1$
 $u_2 = U_i - 10V, i = 0$




$$U_p = U_i \cdot \frac{R_0}{R_i + R_0} = \frac{U_i}{2} = 5V$$

$$U_T = +U_p$$

$$t = \frac{s}{r} = e \cdot \sqrt{L} =$$


$$T = 0,7 \cdot 10^{-9} s$$

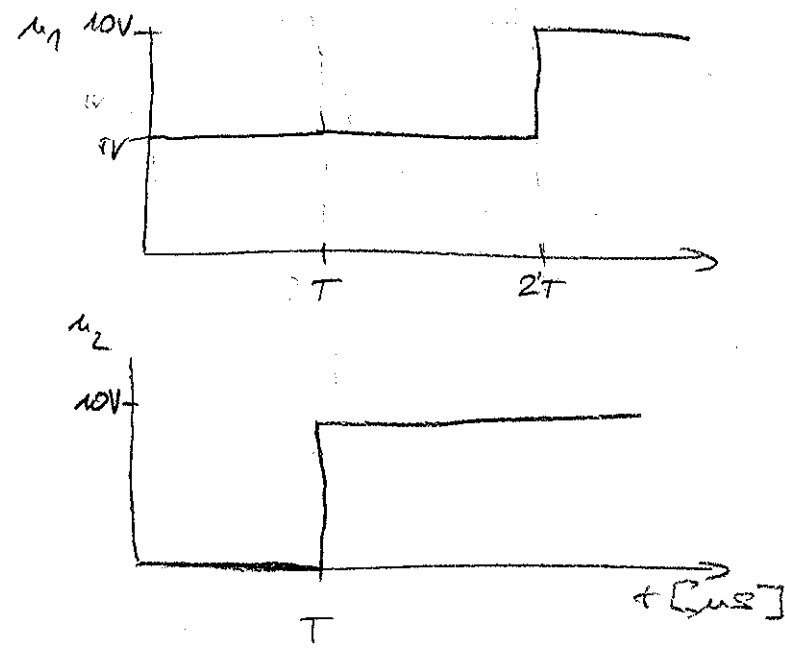

r.p.
r.p. parameter
 $R_s = 0 \rightarrow \beta_{in} = -1$
 $u_2 = 0$

$$U_p = 5V$$

$$U_T = -5V$$

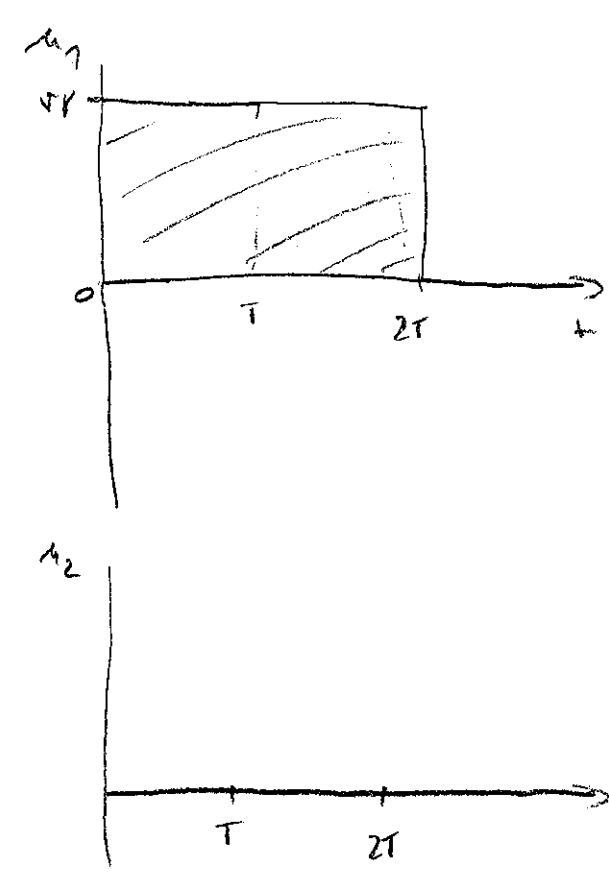


$T. 11$
 $L = 0,1 \cdot 10^{-6} \text{ H} \cdot \text{m}^{-1}$
 $C = 10 \cdot 10^{-12} \text{ F} \cdot \text{m}^{-1}$
 $U_{i0} = 10 \text{ V}$
 $R = 100 \Omega$
 $R_s = 3R_0$

$$U_p = U_{i0} \cdot \frac{R_0}{R_s + R_0} = 5 \text{ V}$$

$$U_z = U_p \cdot \frac{R_2 - R_0}{R_s + R_0} = 2,1 \text{ V}$$

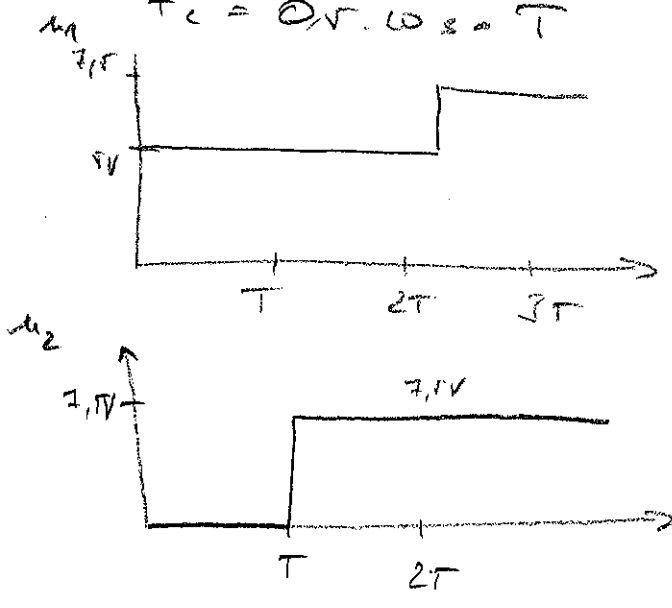
$$t_c = 0,1 \cdot 10^{-6} \text{ s} = T$$



$T. 10.$
 $L = 0,1 \cdot 10^{-6} \text{ H} \cdot \text{m}^{-1}$
 $C = 10 \cdot 10^{-12} \text{ F} \cdot \text{m}^{-1}$
 $U_{i0} = 10 \text{ V}$
 $R = 100 \Omega$
 $R_s = R_0 \Rightarrow P_s = 0$

$$U_p = U_{i0} \cdot \frac{1}{2} = 5 \text{ V}$$

$$U_z = U_p \cdot 0 = 0 \text{ V}$$

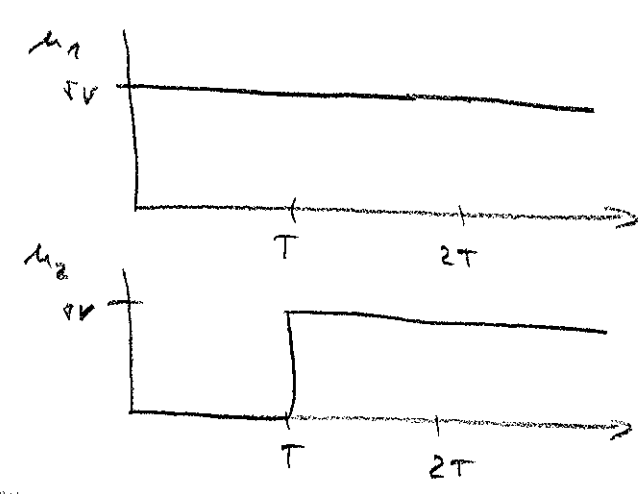

$T. 12$
 $L = 0,1 \cdot 10^{-6} \text{ H} \cdot \text{m}^{-1}$
 $C = 10 \cdot 10^{-12} \text{ F} \cdot \text{m}^{-1}$
 $U_{i0} = 10 \text{ V}$
 $R = 100 \Omega$
 $R_s = \frac{1}{3} R_0$

$$U_p = U_{i0} \cdot \frac{1}{3} = 3,33 \text{ V}$$

$$U_z = U_p \cdot \frac{R_2 - R_0}{R_s + R_0} = U_p \cdot \frac{1}{2} = -1,67 \text{ V}$$

$$T = t_c = L \cdot \sqrt{C} = 0,1 \cdot 10^{-6} \text{ s}$$

