

# Logické systémy

## 1.1. Základní hradla

vstupy	AND	OR	NAND	NOR	XOR	NXOR
x y						
0 0	0	0	1	1	0	1
0 1	0	1	1	0	1	0
1 0	0	1	1	0	1	0
1 1	1	1	0	0	0	1

Karnaughova mapa pro ABCD:

vstup	NOT
x	
0	1
1	0

		AB			
		00	01	11	10
CD	00	$m_0$	$m_4$	$m_{12}$	$m_8$
	01	$m_1$	$m_5$	$m_{13}$	$m_9$
	11	$m_3$	$m_7$	$m_{15}$	$m_{11}$
	10	$m_2$	$m_6$	$m_{14}$	$m_{10}$

Minimalizace v Karnaughově mapě:  
výběr jedniček – součet součinů  
výběr nul – součin součtů

## 1.2. Zákony Boolovy algebry

$$A \cdot (A + B) = A, \quad A + (A \cdot B) = A$$


$$A \cdot (\bar{A} + B) = A \cdot B, \quad A + (\bar{A} \cdot B) = A + B$$

• De Morgan:  $A + B = \overline{\bar{A} \cdot \bar{B}}, \quad A \cdot B = \overline{\bar{A} + \bar{B}}$   
 $A + B + C + D + \dots = \overline{\bar{A} \cdot \bar{B} \cdot \bar{C} \cdot \bar{D} \cdot \dots}$

• Consensus:  $AB + \bar{A}C + BC = AB + \bar{A}C$   
 $(A + B)(\bar{A} + C)(B + C) = (A + B)(\bar{A} + C)$

## 1.3. Klopné obvody

### 1.3.1. RS

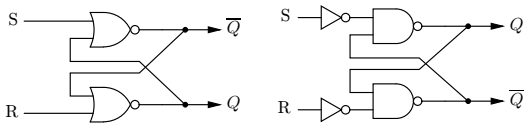

Přechodová tab.

S	R	$Q^+$
0	0	$Q^-$
0	1	0
1	0	1
1	1	$\times$


Budící tab.

Q	$Q^+$	S	R
0	0	0	$\times$
0	1	1	0
1	0	0	1
1	1	$\times$	0

Minimalizace:

$S - 1, 1, \times$ , žádné 0 nebo 0;  
 $R - 0, 0, \times$ , žádné 1 nebo 1;

### 1.3.2. D Latch

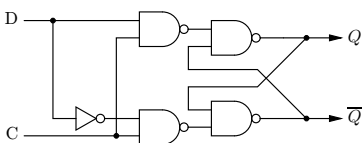


Přechodová tab.

D	C	$Q^+$
0	0	$Q^-$
0	1	0
1	0	$Q^-$
1	1	1

Budící tab.

Q	$Q^+$	D
0	0	0
0	1	1
1	0	0
1	1	1

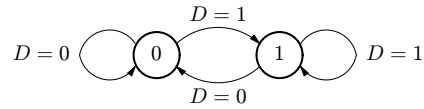

Minimalizace:  $D - 1, 1, \times$ , žádné 0 nebo 0;

### 1.3.3. JK ( $J \sim S, K \sim R$ )


$$Q^+ = J\bar{Q} + \bar{K}Q$$

Přechodová tab.

C	J	K	$Q^+$
$\bar{1}$	0	0	$Q^-$
$\bar{1}$	1	0	1
$\bar{1}$	0	1	0
$\bar{1}$	1	1	$Q^-$
0	$\times$	$\times$	$Q^-$

Budící tab.

Q	$Q^+$	J	K
0	0	0	$\times$
0	1	1	$\times$
1	0	$\times$	1
1	1	$\times$	0

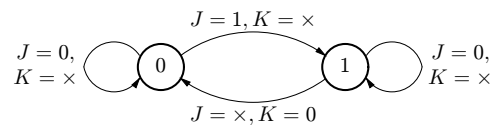


Minimalizace:

$J -$  všechny 1, některé 0, 1,  $\times$ ;  
 $K -$  všechny 0, některé 1, 0,  $\times$ ;

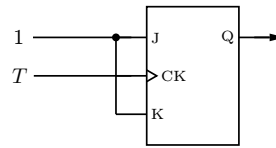
### 1.3.4. T flip-flop

$$Q^+ = T \oplus Q = T\bar{Q} + \bar{T}Q$$



Budící tab.

Q	$Q^+$	T
0	0	0
0	1	1
1	0	1
1	1	0

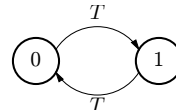

Minimalizace:

$T - 0, 1, 1$ , žádné 0, 1

## 1.4. Boolovská diference

$$\frac{dF(x)}{dx_i} = F(x_1, \dots, x_i, \dots, x_n) \oplus F(x_1, \dots, \bar{x}_i, \dots, x_n)$$

$$\frac{dF(x)}{dx_i} = \frac{dF(x)}{dx_i}, \quad \frac{dF(x)}{dx_i} = \frac{dF(x)}{d\bar{x}_i}$$

$$\frac{d(F(x) \cdot K)}{dx_i} = K \frac{dF(x)}{dx_i}, \quad \frac{d(F(x) + K)}{dx_i} = \bar{K} \frac{dF(x)}{dx_i}$$

$$\frac{d(K + x_i K_1 + \bar{x}_i K_0)}{dx_i} = \bar{K}(K_1 \oplus K_0)$$

Detekce poruchy:

$x_i/0$  získáme řešením  $x_i \frac{dF}{dx_i}$ ,  
 $x_i/1$  řešením  $\bar{x}_i \frac{dF}{dx_i}$

## 1.5. Vlastnosti nonekvivalence (XOR, $\oplus$ )

$$F \oplus G = F\bar{G} + \bar{F}G$$

$$F \oplus F = 0, \quad F \oplus \bar{F} = 1$$

$$F \oplus 1 = \bar{F}, \quad F \oplus 0 = F$$

$$FG \oplus FH = F(G \oplus H)$$

$$F + G = F \oplus G \oplus FG$$

$$\bar{F} \oplus \bar{G} = \bar{F} \oplus G = F \oplus \bar{G}$$

$$F \oplus G = H \Rightarrow F \oplus H = G, G \oplus H = F$$