

Color Computer SSTV: Part I

*Turn your CoCo into a complete SSTV terminal!
How? First, build this high-resolution display system.*

Clayton W. Abrams K6AEP
1758 Comstock Lane
San Jose CA 95124

Dr. Ralph A. Taggart WB8DQT
602 Jefferson Street
Mason MI 48854

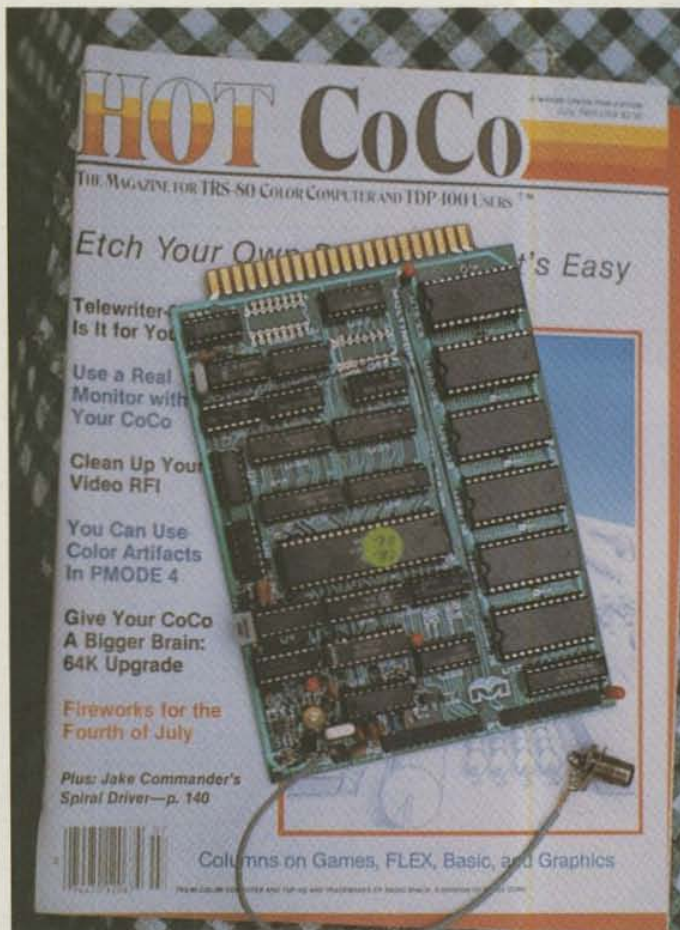


Photo A. Multimode display board, showing the physical size of a production display interface. The board has 16K of display memory.

This two-part article describes a high-resolution television display system for the Radio Shack Color Computer® (CoCo). This system provides the CoCo computer with more display capability than any low-cost computer. You might ask why you

should use your CoCo to display and generate television images. One answer is, for communications.

Imagine taking your CoCo with a hardware-software interface and connecting it to amateur-radio equipment and transferring a picture to

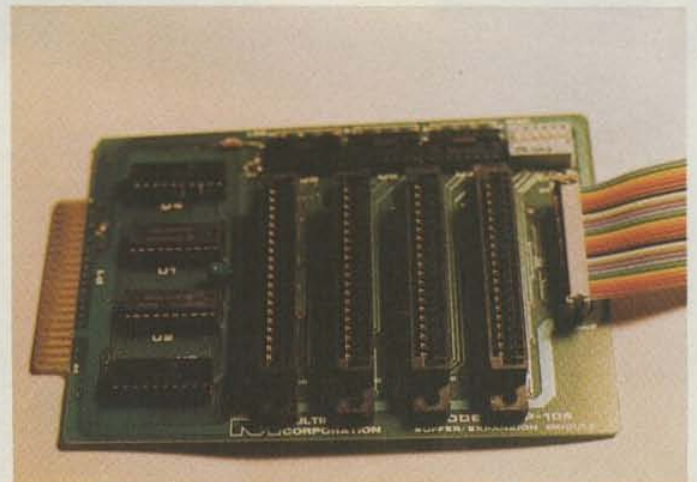


Photo B. Multimode CoCo interface board, which plugs into the expansion interface of the CoCo. A 26-pin flat cable interconnects the interface board and the display board.

someone miles away, or receiving weather-satellite pictures. The digital-television-display field is one which has not been explored by the amateur-computing community, and only a small amount of commercial equipment exists for such applications. In this article, instructions will be provided to construct a card to display high-resolution images and provide interfaces to receive weather-satellite pictures or amateur-radio SSTV.

Before plowing ahead with a lot of technical jargon and confusing terms, some definitions are in order.

Background

In display terminology two terms are particularly important. These terms are used also in television. The first is pixel, and it relates to the smallest element of a picture which can be seen on the TV screen. In normal TV, the pixels are so small that they tend to blend together to form a contiguous image. In digital TV, a pixel is a unit in the picture which can be seen by the unaided eye. Each pixel in digital TV has an intensity or discrete color. The main goal in digital TV is to place the most pixels on a line to form the smoothest image. To do this as well as standard TV does takes a lot of complex and costly circuitry.

The second term is number of lines per picture. In the USA, standard TV has 262 lines per frame or 525 lines per interlaced picture. In digital TV, the number of lines is often reduced from normal TV for cost and simplicity reasons.

If a digital-display system could be developed around a standard microprocessor system, the system would be very versatile. The few commercial display systems which have been developed to date have some disadvantages.

Expandability. Micropro-

cessors have been installed in some of the new display-system designs. All of these units are not user-programmable. Most vendors would rather provide users with new units when their function is to be expanded. If a system were to be based on a commercial microprocessor with a good software base, the system could be expanded as technology progresses.

Fixed Architecture. Most commercial systems are built around a large planar board with lots of ICs and discrete components. These units are designed for a specific application and a limited life span. Adding interfaces like FAX and other applications is difficult. For this reason, the modular approach of functional units connected to a microprocessor makes good sense.

Up to a few years ago, digital TV was not possible. With the explosion of the semiconductor industry, the price of ICs has fallen to a level which makes this economically possible. Most of the early digital TV scan converters used were hardware-only devices. These units were very dumb and

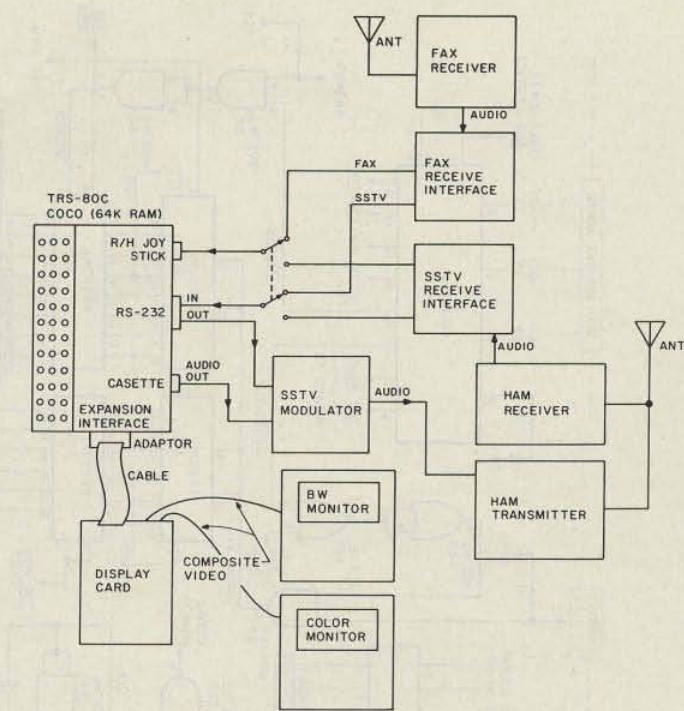


Fig. 1. System block diagram, showing the interconnection of the computer and all the interfaces.

could only generate and display images. The explosion of digital computers and the incorporation of digital displays in computers makes the whole concept very exciting. Once an image is placed in the computer, almost anything is possible: communications, image analysis by computer for manufacturing inspec-

tion, medical applications, or art forms for their own sake.

Two applications will be described in this article. The first application is amateur-radio slow-scan television; the second is weather-satellite reception. While the applications are similar in that they require some means of picture displaying and a

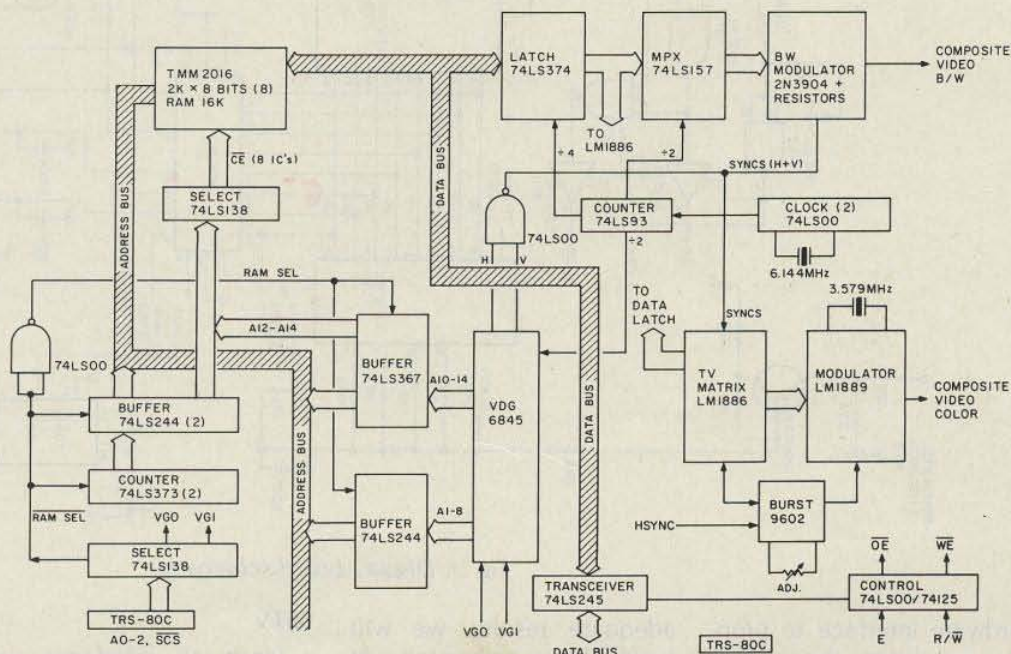


Fig. 2. Display block diagram, showing how the display interface functions. Only the important ICs are shown.

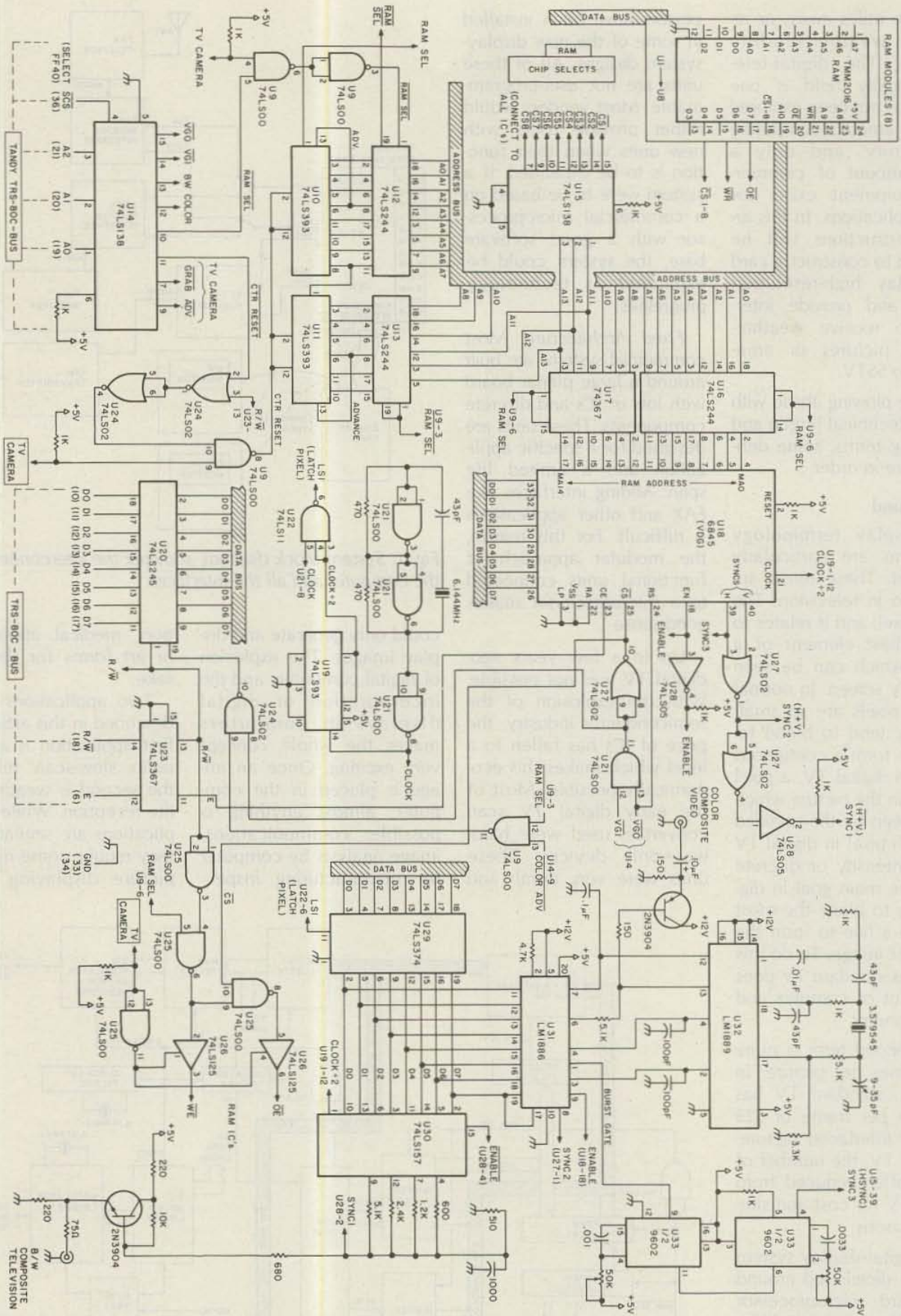


Fig. 3. Display board schematic.

hardware interface to properly condition the signal, and each requires trade-offs and compromises to achieve

adequate results, we will treat them separately in order to do an adequate job on each.

SSTV

Since all interfaces use simple hardware, the heart of the system is software. It

would be impossible to publish an entire software package in an article of this type. To date, thousands of lines

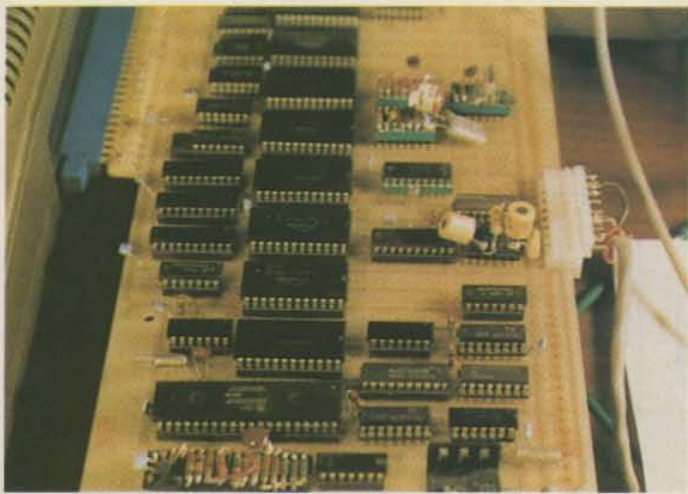


Photo C. The prototype board by K6AEP was one of the first display boards constructed. The board is plugged into a CoCo. The board was point-to-point wired and is exactly like the schematic in Fig. 3. All of these photos in part I of this article were generated by this board. The same results can be achieved by the commercial display boards.

of code have been developed. What will be provided here is a technical description of how the software and hardware interfaces function and the steps necessary to develop code. You will find it possible to modify the concepts we present for interfacing with any microprocessor system.

The Display Criteria

Since the main goal of the display card is to produce quality images, it is important to make the picture density as high as possible. This requires the addition of RAM memory in which the image will be saved and displayed. Experimentation by many people over a period of years has determined that a minimum of 128 pixels per line is required for low-resolution images, with at least 16 gray levels. Some experimentation which I conducted in mid-1982 indicated that a minimum of 256 colors per pixel is required to display low-resolution color-TV images.

Armed with this information, a design criteria of 256 pixels per line, 16 gray levels, on 128 lines was defined for black and white displays. This equates to a display size of 16K of dis-

play RAM. With a little clever programming and slight reconfiguration of data bits, a total of 256 colors can be displayed for each pixel with 128 pixels per line on 128 lines.

Obviously, a system can be constructed with higher resolution, but as the digital-display density increases so do the cost and complexity. Since this project was created for the average hobbyist with a limited budget, the above criteria seem adequate for today's technology.

Hardware Design

It is unfortunate that no off-the-shelf module or design provides the necessary ingredient to display TV-type images. Many manufacturers have developed display-controller ICs for computer terminals, but in most cases they are unusable in TV applications. One of the few ICs which make the job easier is the Motorola 6845. This IC is the heart of the display board and causes the image to be displayed.

The card is designed to attach to the Radio Shack TRS-80C Color Computer, but the design concept is so basic that it can be altered to attach to any microcom-

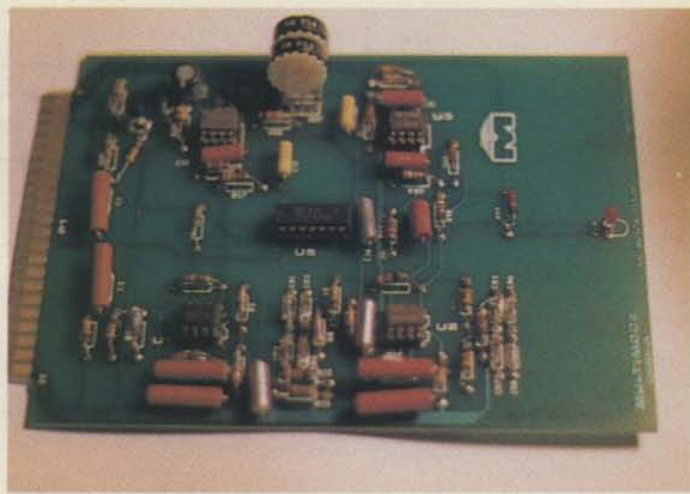


Photo D. A multimode SSTV receive interface. This board is a commercial version of the SSTV receive interface. The physical size is the same as the display board.

puter. The card functions by first generating or placing an image in the main memory of the computer. The TV image can be received through a slow-scan demodulator attached to the receiving equipment then connected to the joystick input of the computer.

Another method of image generation is to attach a special hardware interface to the display card and frame-grab the image into the display card from a TV camera. At this time the TV-camera interface has not been developed. When using the TV camera, the image will be loaded into the video card first and then transferred by computer software to main memory.

System Description

Fig. 1 provides a block diagram of the entire system. The TRS-80C in this application acts as an intelligent controller. All interfaces are very primitive and cannot function without intensive control from the computer. When an image is to be displayed from the receiver, the audio tones are first detected by the display demodulator and converted to two types of signals: sync pulses and a dc voltage which changes as a function of the input audio frequency. These signals are

connected to the CoCo's RS-232 input and the joystick input.

The joystick input is actually an analog-to-digital converter which can be used to digitize slow-scan TV video into picture information. All of the operation is controlled by software in the CoCo. When digitized, the pixels are transferred to the display card and immediately displayed. For transmission, the image is first created by software and placed in the CoCo's memory. To transfer the image to a transmitter, the sync pulses are controlled by the RS-232 output line and the video is controlled by the computer's cassette output, which is a digital-to-analog converter.

The above process is true only for black and white television. Color digital TV is more complex. Color TV is developed or transferred from three image planes. Each plane consists of the three prime colors (red, green, and blue). When the three frames are mixed together, a color image is formed. The image can then be transferred to the display card. The transmission method of colored television is either by frame-sequential or by a colored line-sequential multiplexed method.

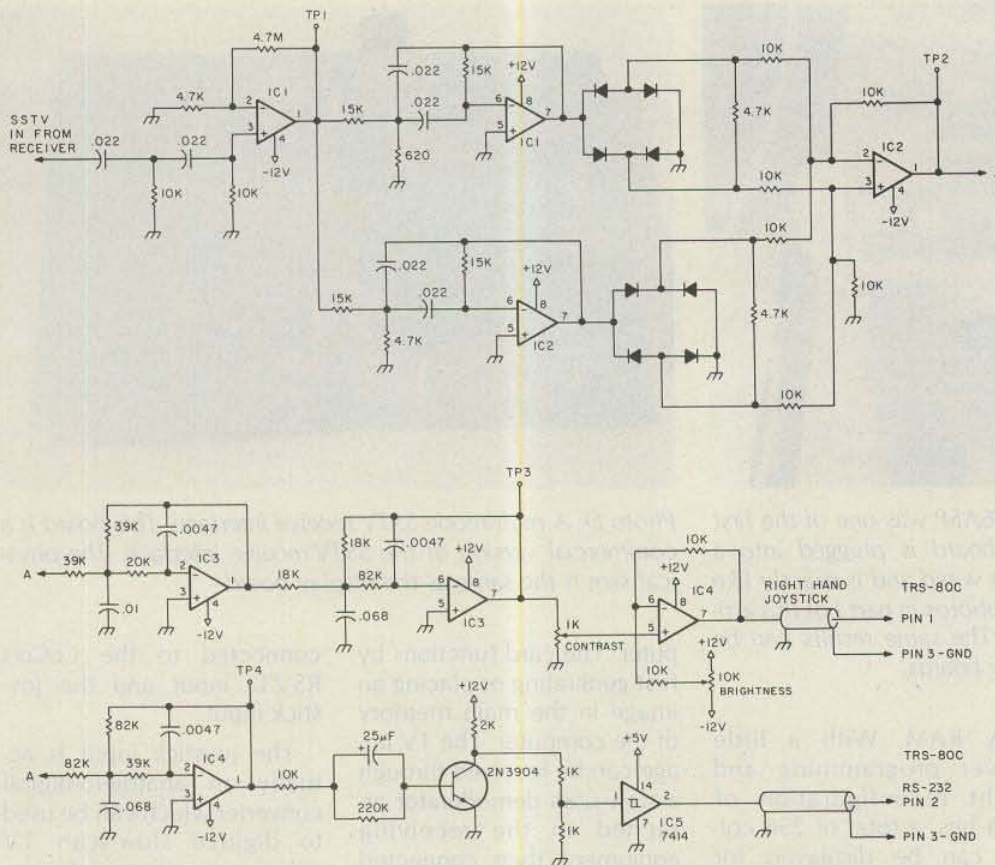


Fig. 4. SSTV/FAX receive demodulator schematic showing a front end which can be used with the computer to display both SSTV and FAX images. The FAX application can be used only on the HF bands.

The block diagram of the display card is shown in Fig. 2 and the schematic is shown in Fig. 3. The following sections describe the major functional parts of the display board.

Display Board

The display board is attached to the expansion port on the side of the CoCo. This port provides connection to the address, data, and control signals of the 6809E

MPU. Wiring to the CoCo must be as short as possible; less than one-half-inch leads are a must. The data lines are connected to both the eight RAM ICs and the VDG U18 (6845) display-controller IC through a data bus transceiver (U20). The R-W line determines if the CPU is reading or writing to the board.

In order for the display-controller IC to function, you must first write data to

its 18 internal registers. Only three address bits of the 6809 CPU IC are connected to the card. These low-order address bits select the mode which you are performing. The SCS line on the TRS-80C connector is used to select address FF40. The interface E line is the enable signal from the 6809 CPU. This line is used to synchronize the 6845 to the CPU IC for writing to its internal registers.

1. *Functional Selection.* All internal functions of the card are software-selected by a U14 (74LS138). The functions are shown in

Table 1 and are described in more detail in the programming section of this article.

2. *Random Access Memory.* This card contains 16K of display RAM (U1 to U8) in eight 2K-by-8-bit ICs. Static RAM was used so as to make the design as simple as possible. Dynamic RAM has the advantage of lower cost but requires extra circuitry to develop RAS and CAS signals, and it is difficult to correct and diagnose problems when they occur. Simple changes can be made to the circuit to add more display memory. Modifications have been made to add 32K RAM. The board can then display 256 pixels on 256 lines, black and white. Television pictures in this mode are starting to approach standard US TV quality pictures.

Control of read or write to the RAM is determined by U25 and U26. During most of the time, RAM is in the read mode. This causes the video data to be valid on the internal data bus. When data is written, it is transferred to and from the CoCo through bus transceiver U20 to the RAM ICs.

3. *Video Display Generator.* The VDG U18 is the heart of the display board. This integrated circuit has 18 registers. In order to make the board operational, the registers must be pre-loaded before a picture can be displayed on the card. This IC is used to develop the video refresh timings of the RAM. By simply changing the initialization values, either 50-Hz or 60-Hz video can be displayed.

An example of CRT initial-

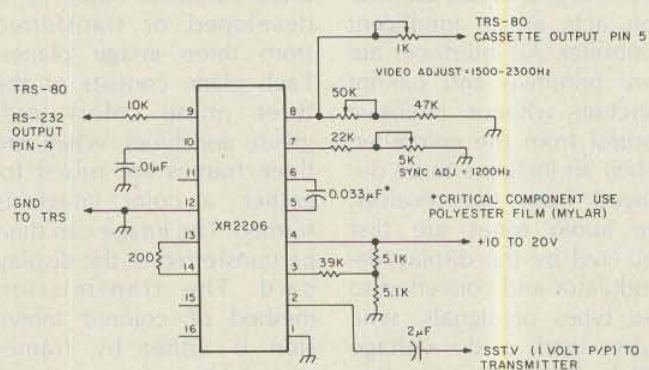


Fig. 5. SSTV modulator, used to transmit SSTV pictures on the HF amateur bands.

ADDRESS SIGNAL

FF40	VG0 VDG controller address register
FF41	VG1 VDG controller data register
FF42	Spare
FF43	Spare
FF44	Reset—reset RAM address counter
FF45	Select—send picture data to card
FF46	Frame Grab—TV camera—reserved
FF47	Color—TV camera—reserved

Table 1.

* ASSEMBLER EXAMPLE FOR CODING A PROGRAM
 * TO RECEIVE SSTV OF FAX WITH A TRS-80C
 * COLOR COMPUTER
 *

```

0600          OPT PAG
              ORG #0600
* EQUATES
FF45 PORT2 EDU #FF45  DISPLAY A PIXEL
FF44 PORT3 EDU #FF44  RESET HARDWARE COUNTER
1000 START EDU #1000  DUMMY START ADDRESS FOR PICTURE INFO

0600 0E 1000  RECV  LDX #START  START OF PICTURE IN RAM
0603 0D 09    BSR INIT      INITIALIZE MPX IN TRS-80C
0605 06 00    LDA #120      256 PIXELS PER LINE
0607 07 0651  STA PIXC      PIXEL COUNTER
060A 07 0652  STA LINE      LINE COUNTER
060D 07  FF44  STA PORT3    RESET COUNTER ON DISPLAY CARD
*
0610 0D 30    BSR VSYNC     WAIT FOR VERT SYNC
0612 0D 37    RECV1 BSR ADC      GET A READING FROM COCD ADC
0614 12      NOP            EQUALIZE CYCLES TO KEEP
0615 12      NOP            SOFTWARE JITTER TO A
0616 12      NOP            MINIMUM
0617 12      NOP
0618 12      NOP
0619 12      NOP
061A 34 02    PSHS A        SAVE ADC ON THE STACK
061C 10BE 064F LDY DELAY     PLACE DELAY CONSTANT IN Y
0620 31 3F    RECV2 LEAY -1,Y  DELAY LOOP BETWEEN PIXELS
0622 26 FC    BNE RECV2
0624 44      LSR          FORMAT PIXEL INTO RIGHT
0625 44      LSR          NIBBLE (4 BITS)
0626 44      LSR
0627 44      LSR
0628 AA E0    ORA #,S+     ADD PIXELS
062A 10BE 064F LDY DELAY     DELAY CONSTANT
062E 07 FF45 STA PORT2    DISPLAY TWO PIXELS
0631 A7 00    STA #,X+     PLACE A COPY IN RAM
0633 31 3F    RECV3 LEAY -1,Y  DELAY LOOP
0635 26 E9    BNE RECV2
0637 7A 0651 DEC PIXC      DECREMENT PIXEL COUNTER
063A 06 09    LDA #120      RE-INT PIXEL COUNTER
063C 07 0651 STA PIXC
063F 26 D1    BNE RECV1
0641 7A 0652 DEC LINE     DO IT TILL LAST PIXEL
0644 27 04    BEQ END      IS IT LAST LINE ?
0646 0D 04    BSR HSYNC     DO IT TILL LAST LINE
0648 20 CB    BRA RECV1    WAIT FOR HORIZONTAL SYNC
*
* END THE WHOLE PROCESS
064A 39      END RTS        RETURN TO MAIN LINE CALL
*
* ADC ROUTINE- RECEIVE A PIXEL THROUGH ADC PORT
* JOYSTICKS - PERSERVE THE X AND A REGISTERS
* RETURN WITH ADC VALUE IN A
064B 39      ADC RTS        DUMMY RETURN
*
* SYNC ROUTINES- SAMPLE RS-232 INPUT PORT AND WAIT FOR
* THE INPUT TO RISE THAN FALL. VERTICAL SYNC SHOULD
* LOOK ONLY FOR PULSES GREATER THAN APPROXIMATELY 30
* MILLISECONDS. IF THE PULSE WIDTH IS LESS THAN APPROX.
* 3 MILLISECONDS THEN IT IS A HORIZONTAL SYNC PULSE.
064C 39      HSYNC RTS      DUMMY H SYNC
064D 39      VSYNC RTS      DUMMY V SYNC
*
* INITIALIZE MULTIPLEXER IN COCD TO CONNECT JOYSTICK
* INPUT TO THE CORRECT PIN ON THE CONNECTOR. JOYSTICK
* INPUTS CAN BE A POSSIBILITY OF 4 PINS
064E 39      INIT RTS        DUMMY MPX SELECTION
*
* DELAY- CONSTANT TO ALLOW FOR DELAY BETWEEN PIXELS
* VARIABLE TO COVER ALL MODES OF RECEPTION
064F 0010    DELAY FDB #0010  SAMPLE DELAY
*
* GENERAL STORAGE FOR PROGRAM CONSTANTS
0651 00      PIXC FCB 0      PAXLE COUNTER DELAY
0652 00      LINE FCB 0     LINE COUNTER DELAY
*
* END RECV

```

Fig. 6. Program example for SSTV/FAX receive, written in 6809 assembler language, to demonstrate how easily a receive routine can be written. The routine cannot be executed without software additions.

ization is contained in the programming section. The initialization constants were chosen to display an image with the minimum amount of tearing and proper centering on a 9-inch RCA Color Trak TV set. The TV set was interfaced to the video card by a Radio Shack rf modulator.

4. *The Master Clock.* The master clock is a crystal oscillator operating at 6.144 MHz and is generated by a 74LS00 U21 IC. This crystal frequency was chosen to display an active picture time of 42 microseconds.

The initialization software of the 6845 is used to fine-tune this display time. A counter is used to divide the clock frequency by 2 and 4.

5. *The Internal Data and Address Bus.* The entire card is designed to display an SSTV picture continuously. Since the card must be powered by an external source different from the computer, power can be dropped on the computer and the display will still be active.

When a picture is to be displayed on the card, the refresh process is inter-

* ASSEMBLER CODE EXAMPLE OF TRANSMISSION OF
 * A SSTV PICTURE OVER AMATEUR RADIO USING A
 * TRS-80C COLOR COMPUTER
 *

```

0600          OPT PAG
              ORG #0600
* EQUATES
FF45 PORT2 EDU #FF45  DISPLAY A PIXEL
FF44 PORT3 EDU #FF44  RESET HARDWARE COUNTER
1000 START EDU #1000  DUMMY START ADDRESS OF PICTURE INFO
FF20 PIA EDU #FF20   DAC PORT (CASSETTE OUTPUT)

0600 0E 1000  XMIT  LDX #START  START ADDRESS TO XMIT
* FIRST DISPLAY PICTURE ON THE SCREEN
0603 07  FF44  STA PORT3    RESET HARDWARE COUNTER
0606 06 00    XMIT1 LDA #,X+  GET A PIXEL
0608 07  FF45  STA PORT2    DISPLAY IT ON CARD
0609 0C 5000  CMPX #START+4000 LAST BYTE OF DISPLAY ?
060E 26 F6    BNE XMIT1
0610 10BE 0655 LDY #TABLE   ADDRESS OF PIXEL TABLE
0614 7F 0666 CLR LINE     CLEAR LINE COUNTER
0617 7F 0665 CLR PIXC    CLEAR PIXEL COUNTER
061A 0E 1000 LDX #START    START OF PICTURE RAM
061D 0D 33    BSR XVERT     GET A PIXEL
061F A6 00    XMIT2 LDA #,X+  SAVE IT ON THE STACK
0621 34 02    PSHS A
0623 44      LSR          FORMAT PIXELS FOR TRANSMISSION
0624 44      LSR
0625 44      LSR
0626 44      LSR
0627 A6 A6    LDA A,Y
0629 07 FF20 STA PIA        XMIT A PIXEL
062C 35 02    PULS A        GET BACK ORIGINAL TWO PIXELS
062E 04 0F    ANDA #00F    MASK OUT HIGH ORDER NIBBLE
0630 0D 22    BSR DELAY    DELAY LOOP BETWEEN PIXELS
0632 A6 A6    LDA A,Y
0634 07 FF20 STA PIA        XMIT NEXT PIXEL
0637 0D 18    BSR DELAY    DELAY A PIXEL
0639 7C 0665 INC PIXC
063C 06 0665 LDA PIXC
063F 4D      TSTA
0640 26 C4    BNE XMIT1
0642 7F 0665 CLR PIXC
0645 0D 0C    BSR XHORIZ   RESET PIXEL COUNTER
0647 7C 0666 INC LINE     XMIT A HORIZONTAL SYNC
064A 06 0666 LDA LINE     GET NEW LINE COUNT
064D 01 00    CMPA #12B    LAST LINE ?
064F 26 05    BNE XMIT1   NOT LAST LINE
0651 39      RTS          RETURN TO MAIN LINE CALL
*
* XMIT SYNC PULSES - VERTICAL SYNC WILL BE
* 50 MILLISECONDS IN DURATION, THE HORIZONTAL
* SYNC PULSE WILL BE 5 MILLISECONDS IN DURATION
*
0652 39      XVERT RTS     DUMMY ROUTINE
0653 39      XHORIZ RTS    DUMMY ROUTINE
*
* PIXEL DELAY ROUTINE DELAY A SUFFICIENT AMOUNT
* OF TIME BETWEEN PIXELS TO XMIT THE CORRECT
* HORIZONTAL SYNC FREQUENCY
0654 39      DELAY RTS     DUMMY ROUTINE
*
* PIXEL LOOK UP TABLE, CORRECT PIXEL BIT PATTERNS
* WILL BE ACCESSED IN THIS ROUTINE TO PLACE A
* A VOLTAGE ON THE SSTV MODULATOR TO PROVIDE THE
* APPROPRIATE VOLTAGE F=WHITE 2300 HZ.
* B=BLACK 1500 HZ
*
0655      TABLE RMB 16    16 BYTES OF DATA
*
* COUNTERS IN RAM
0665 00      PIXC FCB 0
0666 00      LINE FCB 0
*
* END XMIT

```

Fig. 7. Program example for SSTV transmission.

rupted for a few microseconds. This causes a small white line to appear on the display. The direct memory access (DMA) scheme used on the card is very simple in principle. Normally the addressing of RAM is from the VDG through two tri-state buffers, U16 and U17. When the CPU writes to RAM, not-RAM select is brought low and the RAM address is generated by two counters, U10 and U11. At this time, VDG buffers U12 and U13 are floated on the address bus and the counter buffers drive the bus. After the RAM has been written, the counter advances to the next address.

6. *Display Data.* The digital display data is latched from the data bus at the correct time by the 74LS374

U24; the black and white is twice the rate of the color. The 74LS374 U39 is latched from the data bus every 650 nanoseconds. This data is fed to both the black and white and color modulators. A multiplexer is used to feed the black and white modulator. The multiplexer 74LS157 U30 is clocked at a rate of 325 nanoseconds, which is 256 pixels per line of SSTV.

7. *Black and White Modulator.* The black and white modulator is fed from the multiplexer, U30, which feeds first the 4 low-order bits (nibbles) then the high-order nibble. The output of the multiplexer is connected to a simple digital-to-analog converter (D/A) which consists of a transistor and 10 resistors.

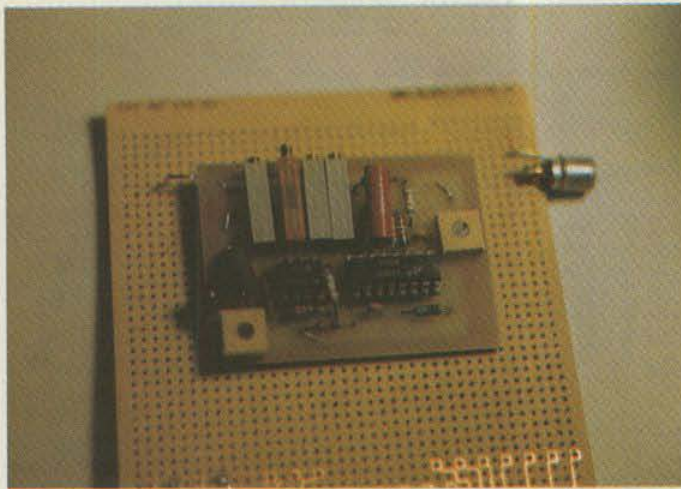


Photo E. RTM Circuit Board's SSTV transmit interface placed on a Tandy prototype card. The card can be plugged into a card cage or a socket for ease of removal and repair.

Sync pulses are generated by the VDG U13, are ORED together by U27, then mixed with video data in the single-transistor D/A converter. Since 4 bits are used, the modulator is restricted to 16 possible gray levels per pixel.

A picture-smoothing capacitor (1000 pF) was placed across the 510-Ohm resistor to ground at the D/A summing point. The value of this capacitor can be optimized to produce the picture most desirable. The absence of the capacitor produces a more digitized picture.

8. Color-SSTV Modulator.

The color-SSTV modulator consists of three ICs, LM1889 U32, LM1886 U31, and a 9602 U33. The SSTV modulator functions by clocking the picture data on the latch. The data is next transferred to the LM1886 which converts the digital pixels to difference and luminance signals. These signals are internally connected to the color modulator which provides composite color video.

Three additional signals are provided to the LM1886, blanking, sync pulse, and a burst gate. The burst gate is developed from a 9602

which is a dual single shot. The burst gate serves as a reference signal. The location of the burst gate must be adjusted to the correct position on the horizontal-blanking back porch. This is the only adjustment on the board.

The digital data to the LM1886 (U32) is in the format of 3-by-3-by-2 bits of red-, green-, blue-frame information. For example, the lower three bits of the byte are the red-frame information, the next three bits are for the green frame, and the most significant bits are for the blue frame.

This configuration allows for a possible 256 combinations which are unique colors. Since the LM1886 allows for nine bits of digital data to be inputted, the LSB is tied to the MSB of the blue-frame input of the IC to make the bit pattern compatible with the eight-bit display-data bus. This trick allows for black and white images to be displayed. Without this modification, the black and white images would have a blue hue.

9. TV-Camera Interface. A number of points are identified in the logic of the display-board interface for the inclusion of a TV camera at a later date. The camera interface will function as follows: When the 74LS00 U9-5 is brought low, the counter will drive the address bus. The TV-camera pixel counter will be incremented by the input U9-9. The RAM read/write is controlled by U26, and the TV-camera input at U25-12/13 will cause the RAM to switch to the write mode. Pixels can next be written to the RAM from the data bus.

Receive Demodulator

The receive demodulator is a device which decodes the SSTV tones into a dc voltage proportional to input frequency and digital sync pulses. This circuit converts video tones of 1500 Hz and 2300 Hz to 0 volts and 5

volts, respectively. A frequency of 1200 Hz converts to a positive digital pulse.

The circuit consists of four stages of filtering and one stage of pulse shaping. Its schematic is shown in Fig. 4.

The decode by this circuit is not only compatible with SSTV but can also be used to decode FAX pictures transmitted commercially on the HF frequencies.

The SSTV video enters the demodulator through the limiter circuit, U1. The limiter is connected to two bandpass filters, U1 and U2, which have bandpasses of approximately 1100 to 2400 Hz. These filters are connected to two diode-discriminator circuits which are combined into a differential amplifier. The signal at TP2 is the carrier frequency of the audio signal with amplitude modulation. The signal in this path with TP3 (U3 and U4) is a series of bandpass amplifiers which allow only the video components of 1500 and 2300 Hz to be passed.

The path of TP4 and U4 is used for the detection and waveshaping of the sync signals. The Schmitt trigger, 7414, is used to develop fast rise times of the sync signals and to produce TTL-level voltages. The sync output from the circuit contains both horizontal and vertical sync pulses.

Modulator Circuit

The modulator interfaces to the CoCo and is the circuit which produces the SSTV audio tones for the transfer of video information in computer memory. The interface, shown in Fig. 5, connects to the CoCo through the RS-232 and cassette-output ports. The cassette-output port is a 6-bit digital-to-analog converter.

The circuit functions as follows. When the RS-232 output is raised, the modulator outputs a sync frequency of 1200 Hz. To generate video tones, a ground

```

* ASSEMBLER CODE EXAMPLE TO INITIALIZE THE CRT
* CONTROLLER TO THE APPROPRIATE RATES OF STANDARD
* USA 525 LINE TV AND NTSC COLOR TV
* SLIGHT MODIFICATIONS WILL ALLOW FOR 50 HZ
* 625 LINE AND PAL COLOR
*
      OPT PAB
      ORG $0600

@600
@605 5F      INCRT CLR8
@601 30      BD @00E  LEAX CONCRT,PCR CRT INITIALIZATION CONSTANTS
@605 F7      FF40    INCRT1 STB PORT SELECT REGISTER ADDRESS IN 6845
@608 A6      00      LDA @,X+ GET FIRST CONSTANT
@60A B7      FF41    STA PORT1 PUT DATA INTO REGISTER
@60D 5C      INCB   POINT TO NEXT REGISTER
@60E C1      10     CMPB #16 LAST BYTE ?
@610 26      F3     BNE INCRT1 DO IT AGAIN
@612 39      RTS

      FF40    PORT EQU #FF40 CRT CONTROLLER ADDRESS PORT
      FF41    PORT1 EQU #FF41 CRT CONTROLLER DATA PORT
*
* CRT CONTROLLER IC EQUATES
CONCRT FCB #C0 REG 1 HORIZ TOTAL
        FCB 128 REG 2 CHAR/ROW
        FCB #92 REG 3 HSYNC POSITION
        FCB #1E REG 4 HSYNC WIDTH
        FCB #79 REG 5 VERT TOTAL
        FCB #35 REG 6 VERTSYNC ADJ
        FCB #7F REG 7 CHAR ROWS/FRAME
        FCB #01 REG 8 VSYNC POS
        FCB 0 REG 9 INTERLACE MODE
        FCB 1 REG 10 SCAN LINES/ROW
        FCB 0 REG 11 CURSOR START
        FCB 0 REG 12 CURSOR END
        FCB 02 REG 13 MSB START VIDEO
        FCB 0 REG 14 LSB STOP VIDEO
        FCB 0 REG 15 MSB L/P
        FCB 0 REG 16 LSB L/P
*
      END

```

Fig. 8. Initialization of the display board; this is an example of how the display board 6845 can be initialized.

NEW!

uniden®

Bearcat®

Products

Communications Electronics,™ the world's largest distributor of radio scanners, is pleased to announce that Bearcat brand scanner radios have been acquired by Uniden Corporation of America. Because of this acquisition, Communications Electronics will now carry the complete line of Uniden Bearcat scanners, CB radios and Uniden Bandit™ radar detectors. To celebrate this acquisition, we have special pricing on the Uniden line of electronic products.

Bearcat® 300-E

List price \$549.95/CE price \$339.00
7-Band, 50 Channel • Service Search • No-crystal scanner • AM Aircraft and Public Service bands • Priority Channel • AC/DC
 Bands: 32-50, 118-136 AM, 144-174, 421-512 MHz. The Bearcat 300 is the most advanced automatic scanning radio that has ever been offered to the public. The Bearcat 300 uses a bright green fluorescent digital display, so it's ideal for mobile applications. The Bearcat 300 now has these added features: Service Search, Display Intensity Control, Hold Search and Resume Search keys. Separate Band keys to permit lock-in/lock-out of any band for more efficient service search.

Bearcat® 20/20-E

List price \$449.95/CE price \$269.00
7-Band, 40 Channel • Crystalless • Searches AM Aircraft and Public Service bands • AC/DC Priority Channel • Direct Channel Access • Delay
 Frequency range 32-50, 118-136 AM, 144-174, 420-512 MHz. Find an easy chair. Turn on your Bearcat 20/20 and you're in an airplane cockpit. Listening to all the air-to-ground conversations. Maybe you'll pick up an exciting search and rescue mission on the Coast Guard channel. In a flash, you're back on the ground listening as news crews report a fast breaking story. Or hearing police and fire calls in your own neighborhood, in plenty of time so you can take precautions. You can even hear ham radio transmission, business phone calls and government intelligence agencies. Without leaving your easy chair. Because you've got a Bearcat 20/20 right beside it.

The Bearcat 20/20 monitors 40 frequencies from 7 bands, including aircraft. A two-position switch, located on the front panel, allows monitoring of 20 channels at a time.

Bearcat® 210XL-E

List price \$349.95/CE price \$209.00
6-Band, 18 Channel • Crystalless • AC/DC
 Frequency range 32-50, 144-174, 421-512 MHz. The Bearcat 210XL scanning radio is the second generation scanner that replaces the popular Bearcat 210 and 211. It has almost twice the scanning capacity of the Bearcat 210 with 18 channels plus dual scanning speeds and a bright green fluorescent display. Automatic search finds new frequencies. Features scan delay, single antenna, patented track tuning and more.

Bearcat® 260-E

List price \$399.95/CE price \$249.00
8-Band, 16 Channel • Priority • AC/DC
 Frequency range 30-50, 138-174, 406-512 MHz. Keep up with police and fire calls, ham radio operators and other transmission while you're on the road with a Bearcat 260 scanner. Designed with police and fire department cooperation, its unique, practical shape and special two-position mounting bracket makes hump mounted or under dash installation possible in any vehicle. The Bearcat 260 is so ruggedly built for mobile use that it meets military standard 810c, curve y for vibration rating. Incorporated in its rugged, all metal case is a specially positioned speaker delivering 3 watts of crisp, clear audio.

NEW! Bearcat® 201-E

List price \$279.95/CE price \$179.00
9-Band, 16 Channel • Crystalless • AC only Priority • Scan Delay • One Key Weather
 Frequency range 30-50, 118-136 AM, 146-174, 420-512 MHz. The Bearcat 201 performs any scanning function you could possibly want. With push button ease, you can program up to 16 channels for automatic monitoring. Push another button and search for new frequencies. There are no crystals to limit what you want to hear.

NEW! Bearcat® 180-E

List price \$249.95/CE price \$149.00
8-Band, 16 Channel • Priority • AC only
 Frequency range: 30-50, 138-174, 406-512 MHz. Police and fire calls. Ham radio transmissions. Business and government undercover operations. You can hear it all on a Bearcat 180 scanner radio. Imagine the thrill of hearing a major news event unfold even before the news organizations can report it. And the security of knowing what's happening in your neighborhood by hearing police and fire calls in time to take precautions. There's nothing like scanning to keep you in-the-know, and no better way to get scanner radio performance at a value price than with the Bearcat 180.

Bearcat® 100-E

The first no-crystal programmable handheld scanner. List price \$449.95/CE price \$234.00/SPECIAL!
8-Band, 16 Channel • Liquid Crystal Display Search • Limit • Hold • Lockout • AC/DC
 Frequency range: 30-50, 138-174, 406-512 MHz. The world's first no-crystal handheld scanner has compressed into a 3" x 7" x 1 1/4" case more scanning power than is found in many base or mobile scanners. The Bearcat 100 has a full 16 channels with frequency coverage that includes all public service bands (Low, High, UHF and "T" bands), the 2-Meter and 70 cm. Amateur bands, plus Military and Federal Government frequencies. It has chrome-plated keys for functions that are user controlled, such as lockout, manual and automatic scan. Even search is provided, both manual and automatic. Wow...what a scanner!

The Bearcat 100 produces audio power output of 300 milliwatts, is track-tuned and has selectivity of better than 50 dB down and sensitivity of 0.6 microvolts on VHF and 1.0 microvolts on UHF. Power consumption is kept extremely low by using a liquid crystal display and exclusive low power integrated circuits.

Included in our low CE price is a sturdy carrying case, earphone, battery charger/AC adapter, six AA ni-cad batteries and flexible antenna. The Bearcat 100 is in stock for quick shipment, so order your scanner today.

Bearcat® DX1000-E

List price \$649.95/CE price \$489.00
 Frequency range 10 kHz to 30 MHz. The Bearcat DX1000 shortwave radio makes tuning in London as easy as dialing a phone. It features PLL synthesized accuracy, two time zone 24-hour digital quartz clock and a built-in timer to wake you to your favorite shortwave station. It can be programmed to activate peripheral equipment like a tape recorder to record up to five different broadcasts, any frequency, any mode, while you are asleep or at work. It will receive AM, LSB, USB, CW and FM broadcasts.


There's never been an easier way to hear what the world has to say. With the Bearcat DX1000 shortwave receiver, you now have direct access to the world.

Uniden® PC22-E

List price \$159.95/CE price \$99.00
 The Uniden PC22 is a 40 channel AM remote mobile CB radio. It's the answer for today's smaller cars which don't always provide adequate space for mounting. Since all the controls are on the microphone, you can stash the "guts" in the trunk. The microphone has up/down channel selector, digital display, TX/RX indicator and external speaker jack. Dimensions: 5 3/4" W x 7 7/8" D x 1 1/2" H. 13.8 VDC, positive or negative ground.

QUANTITY DISCOUNTS AVAILABLE

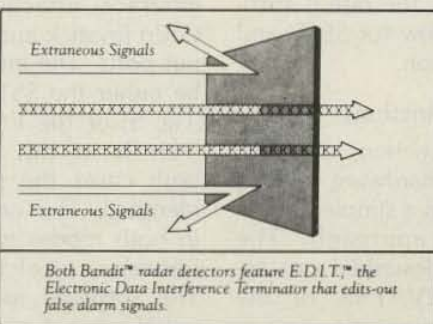Order two scanners at the same time and deduct 1%, for three scanners deduct 2%, four scanners deduct 3%, five scanners deduct 4% and six or more scanners purchased at the same time earns you a 5% discount off our super low single unit price.



Uniden® PC33-E

List price \$59.95/CE price \$44.00
 The Uniden PC33 boasts a super-compact case and front-panel mike connector to fit comfortably in today's smaller cars. Controls: Power & Volume, Squelch; Switches: ANL. Other features of the PC33 include Graduated LED "S"/RF Meter, Digital channel indicator. Dimensions: 6" W x 6" D x 1 7/8" H. ±13.8 VDC.

Uniden® PC55-E

List price \$89.95/CE price \$59.00
 The full featured Uniden PC55 front-panel mike connector makes installation easier when space is a factor. It has ANL, PA-CB, Channel 9 and RF Gain switches. LED "S"/RF meter, TX lite, PA & external speaker jacks. Dimensions: 6" W x 6" D x 1 7/8" H. ±13.8 VDC.

Bandit™ Radar Detectors

Now that everyone else has taken their best shot at radar detection, the Uniden Bandit™ has done them one better...with E.D.I.T.,™ the Electronic Data Interference Terminator that actually edits-out false alarm signals.

The Bandit 55, features a convenient brightness/dimmer control for comfortable day or night driving, plus a handy highway/city control for maximum flexibility wherever you drive. The Bandit 95 Remote, is a two-piece modular unit that lets you mount the long-range radar antenna behind the grill, out of view. The ultra-compact control unit can then be inconspicuously tucked under the dash or clipped to the visor. Order Bandit 55-E for \$119.00 each or the Bandit 95-E Remote for \$139.00 each.

OTHER RADIOS AND ACCESSORIES

FB-E Frequency Directory for Eastern U.S.A. \$12.00
 FB-W-E Frequency Directory for Western U.S.A. \$12.00
 BC-WA-E Bearcat Weather Alert™ \$35.00
 AGO-E Magnet mount mobile antenna \$35.00
 A70-E Base station antenna \$35.00
 Add \$3.00 shipping for all accessories ordered at the same time.
 Add \$3.00 shipping per scanner antenna.

BUY WITH CONFIDENCE

To get the fastest delivery from CE of any product in this ad, send or phone your order directly to our Scanner Distribution Center.™ Michigan residents please add 4% sales tax or supply your tax I.D. number. Written purchase orders are accepted from approved government agencies and most well rated firms at a 10% surcharge for net 10 billing. All sales are subject to availability, acceptance and verification. All sales on accessories are final. Prices, terms and specifications are subject to change without notice. All prices are in U.S. dollars. Out of stock items will be placed on backorder automatically unless CE is instructed differently. A \$5.00 additional handling fee will be charged for all orders with a merchandise total under \$50.00. Shipments are F.O.B. Ann Arbor, Michigan. No COD's. Most products that we sell have a manufacturer's warranty. Free copies of warranties on these products are available prior to purchase by writing to CE. International orders are invited with a \$20.00 surcharge for special handling in addition to shipping charges. Non-certified checks require bank clearance.

Mail orders to: Communications Electronics,™ Box 1002, Ann Arbor, Michigan 48106 U.S.A. Add \$7.00 per scanner, radar detector or CB or \$12.00 per shortwave receiver for U.P.S. ground shipping and handling in the continental U.S.A. For Canada, Puerto Rico, Hawaii, Alaska, or APO/FPO delivery, shipping charges are three times continental U.S. rates. If you have a Visa or Master Card, you may call and place a credit card order. Order toll-free in the U.S. Dial 800-521-4414. In Canada, order toll-free by calling 800-221-3475. WUI Telex CE anytime, dial 671-0155. If you are outside the U.S. or in Michigan dial 313-973-8888. Order today.

Scanner Distribution Center™ and CE logos are trademarks of Communications Electronics.™ Ad # 070184-E † Bearcat is a registered trademark of Uniden Corporation. Copyright © 1984 Communications Electronics

Order Toll Free ... call
1-800-521-4414

COMMUNICATIONS ELECTRONICS™

Consumer Products Division

818 Phoenix □ Box 1002 □ Ann Arbor, Michigan 48106 U.S.A.
 Call TOLL-FREE 800-521-4414 or outside U.S.A. 313-973-8888



Photo F. A color-SSTV picture displayed on a TI color monitor attached to the K6AEP prototype display board. The picture was received over amateur radio on 28.680 MHz by the TRS-80C and saved on tape. The picture was generated by WB0UNB in St. Louis, Missouri.



Photo G. A color-SSTV picture generated by W0LMD and placed on audio cassette tape and loaded into the TRS-80C. This picture shows the effect of color contouring. Since the display has only 256 possible colors, the shading in the flesh-tone regions are noticeable.

potential is applied to both the RS-232 output and the video input. This causes a video frequency of black 1500 Hz to be outputted. When the video level is increased to approximately 1.1 volts by outputting a digital F to the cassette-output port, a frequency of 2300 Hz is generated. By the use of software, an SSTV picture can be generated by software and transmitted.

The Software

The preceding section provides you with a complete description of the hardware requirements for SSTV applications. Obviously, the hardware performs few useful functions without the software. The intent of the hardware design is to place the burden of all timings and control on the software. This allows for the maximum utilization of all hardware interfaces. There are the following limiting factors.

Microprocessor Speed. The reception or transmission of images is limited by the rate at which the instructions can be executed by the CPU. Fortunately, the 6809

microprocessor is very fast due to its rich instruction set and its ability to process 16-bit data even though the processor is on an 8-bit data bus.

Internal Analog-to-Digital Converter. All of the preceding interfaces are based upon the use of the internal analog-to-digital converter in the TRS-80C. This feature is used to process joystick inputs when playing games. The A/D converter uses a simple successive-approximation technique and is driven by the microprocessor. When this technique is used, the conversion rate is quite slow. The tightest loop which can be written to utilize this feature allows for the conversion of 4 bits of data in approximately 75 microseconds. Even though this is slow, the rate is sufficient to allow for SSTV and FAX reception.

Software Functions

In this section, the software and hardware will be described in a simple, broad, overview approach. The principles described can apply to SSTV, FAX, or any other communications mode

which uses a slow rate of transmission or reception. Normally this type of software is called firmware or microcode. Since the software is extremely time-dependent, care must be taken with each instruction written to make the time as short as possible. The description of the software routines will be general enough so that they can be recoded for any general-purpose microprocessor. One important point is that all software must be written in the microprocessor's native assembler language. High-level languages are too slow. Even the most efficient compilers are too slow for SSTV applications.



Receive Software. In Fig. 6 is a simple routine which will receive a picture through an interface attached to the CoCo joystick and RS-232 input ports. The interface can be either the SSTV receiver (Fig. 5) or the FAX receiver (Part II of this article). In both cases the software is identical. The only change in both modes is the delay between pixel reception. The software routines provided are not complete but

they do provide an example to readers ambitious enough to learn assembler-language programming. The program functions as follows.



The first six lines of code initialize program constants for the correct number of lines and place the CoCo multiplexer to the correct joystick-input-connector pin. The hardware counter PORT3 is reset to the upper left-hand corner of the picture area. As soon as a vertical sync signal is received on the interface, the program starts to digitize the picture.

The A/D routine converts the analog input voltage to four digital bits and places this information into the lower nibble of a byte. The byte is next placed on the stack, and a software delay is executed. Upon completion of this delay, the next A/D reading is converted. These two values are next added together on the stack, then placed into RAM, and simultaneously displayed on the video card.

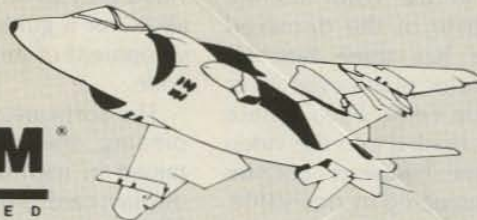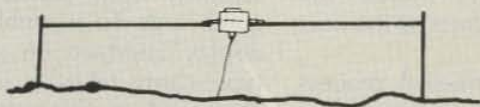The byte in RAM is the same format as the byte on the video card. In the black and white format, the byte



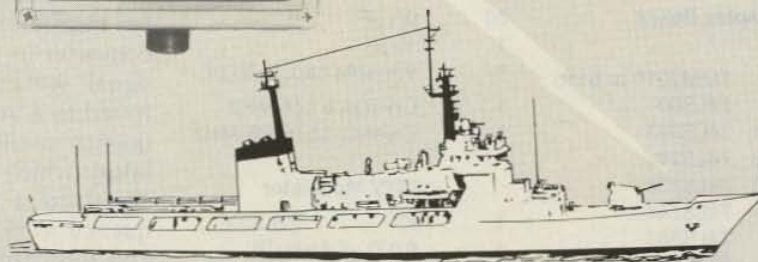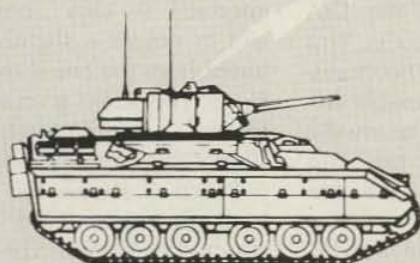MAXCOM
 INCORPORATED
**AUTOMATIC
 ANTENNA MATCHER**



**ONE ANTENNA .3 TO 70 MHZ.
 VSWR 1.5:1 OR LESS**

UNEXCELLED FOR "FREQUENCY HOPPING"

- * NO MOVING PARTS !
- * 5 YEAR WARRANTY !
- * INSTANT MATCHING !
- * 50 OHM INPUT !
- * LOW NOISE !
- * DIPOLE !
- * MARINE !
- * AMATEUR !

- * 100% SOLID STATE !
- * NO CONTROL LEADS !
- * LIGHT WEIGHT !
- * HIGH EFFICIENCY !
- * 200 TO 2KW. P.E.P. !
- * LONG WIRE !
- * MILITARY !
- * AVIONICS !

* NOW IN USE ON THE FOLLOWING NAVY VESSELS *

- * USS ENTERPRISE * USS HECTOR * USS SARATOGA * USS PHOENIX * USS PRAIRIE *
- * USS LEXINGTON, AND US NAVY M.A.R.S. *

**"NEW R.F. GROUNDLESS LONGWIRE MODELS
 NOW AVAILABLE"**

CONTACT

MAGNUM DISTRIBUTORS INC.

1831 South Dixie Highway, Pompano Beach, Florida 33060
 305-785-2002 • Telex 514365 (English FTL)

54

contains two pixels of 4 bits each. In the color format, each byte of the displayed picture has three bits for each color plane except for the blue color. Each time a byte is loaded into the video port, the hardware counter is incremented by one value. This places the DMA address counter to the next location in RAM where the next pixel will be written.

Transmit Software. Fig. 7 contains a simplified example of how an SSTV transmit routine can be written. This example, like SSTV receive,

is very general and is provided only as an example to allow for a guideline for development of more complex code.

The software starts off by placing the picture contained in memory onto the display card. This is accomplished by a simple block move of data to the display card. Prior to the block move, the card hardware counter is reset to zero and 16K bytes are taken from RAM and transferred to the video card. Each time the byte is stored at the video-

card address, the hardware automatically increments the RAM address to the next location.

The transmission process starts off by issuing a vertical sync pulse. This pulse allows for the receiver on the other end of the transmission path to reset the picture to the top of the screen. In the following steps, a picture byte in memory is loaded into the A accumulator. Each nibble is formatted into the lower nibble of a byte. This byte is next used as an offset to a lookup table in memory which will convert the address to an appropriate digital signal which can be transferred to the D/A converter in the CoCo. This signal will then be transferred to a vco (variable frequency oscillator or modulator) which converts this signal to a sinusoidal frequency in the audio range. This resultant signal is SSTV.

The program continues to transmit pixels until 256 pixels are transmitted. At this time a horizontal sync pulse is transmitted. The program next checks if 128 lines have been transmitted. If so the whole process is terminated. If not, the program continues to transmit pixels.

CRT Controller Initialization. Fig. 8 contains a software routine which will initialize the 6845. The routine takes 16 bytes of data in the table CONCRT and stuffs them into the controller registers. This process is accomplished by first presenting the controller register number to the IC. Next the data byte is loaded into the accumulator then transferred to the card.

The display constants in CONCRT are for a standard 60-Hz display system. To revise the formats to 50 Hz, 625 lines, registers 1 and 5 must be changed. The values should be selected by trial and error.

Hardware Construction

The hardware mentioned above can be constructed

on prototype cards or assembled from printed circuit boards. To assemble the display interface on prototype cards takes a lot of work and is vulnerable to errors. Problems experienced with prototyping the card have included: grounds conductors were too small, too few bypass capacitors on power lines, and hardware counters U10 and U11 required a small capacitor on the counter-reset line. Despite these problems, about 5 boards have been constructed to date with excellent results.

Photo A shows the multi-mode display board.¹ This interface is very compact and its design is slightly different from the one shown in Fig. 3. The board is attached to the computer through a short cable (see Photo B).

Photo C shows the original prototype card constructed by K6AEP. The card was point-to-point solder-wired on a prototype SS-50 computer interface card. A small adapter card was constructed to plug into the CoCo expansion interface. (An etched PC board or completely assembled version of this card is available from L. W. InterFace.³)

The SSTV receive and transmit interfaces are available in a number of forms. Photo D shows the multi-mode receive-board interface card; Photo E is a transmit interface from RTM Circuit Boards.²

All boards can be placed in a cabinet with the appropriate power supplies of 5 volts (1 Amp) and ± 12 volts (100 mA). Cables can be made to attach to the computer and receivers.

Part II of this article will describe the FAX hardware.

Conclusions

The computer approach to displaying images is a very cost-effective method. Most alternative methods available are limited in function and are considerably more costly. The commer-

Parts List

Display Board			
ICs		20	0.1 μ F
8 U1-U8	TMM2016 or 6116	1	10 μ F
1 U9	74LS00	1	Variable cap, 9-35 pF
2 U10, U11	74LS393	1	Crystal, 6.144 MHz
2 U12, U13	74LS244	1	Crystal, 3.579545 MHz
2 U14, U15	74LS138		
1 U16	74LS244		SSTV Modulator
1 U17	74LS367	1	IC XR 2206
1 U18	6845	1	0.033 μ F Mylar™
1 U19	744LS93	1	0.01 μ F Ceramic
1 U20	74LS245		
1 U21	74LS00		Resistors
1 U22	74LS11	2	200 Ohms ¼ W, 5%
1 U23	74LS367	2	5.1k ¼ W, 5%
1 U24	74LS02	1	10k ¼ W, 5%
1 U25	74LS00	1	22k ¼ W, 5%
1 U26	74125	1	39k ¼ W, 5%
1 U27	74LS02	1	47k ¼ W, 5%
1 U28	74LS05	1	1k Trimpot
1 U29	74LS374	1	5k Trimpot
1 U30	74LS157	1	50k Trimpot
1 U31	LM1886		
1 U32	LM1889		SSTV Receive Interface
1 U33	9602	4	IC 1-4 MC1458
		1	IC5 7414
Transistors			
2	2N3904		
Resistors			
1	75 Ohms ¼ W, 5%	1	620 Ohms ¼ W, 5%
2	150 ¼ W, 5%	2	1.0k ¼ W, 5%
2	220 ¼ W, 5%	1	2k ¼ W, 5%
2	470 ¼ W, 5%	4	4.7k ¼ W, 5%
1	510 ¼ W, 5%	11	10k ¼ W, 5%
1	600 ¼ W, 1%	3	15k ¼ W, 5%
1	680 ¼ W, 5%	2	18k ¼ W, 5%
8	1k ¼ W, 5%	1	20k ¼ W, 5%
1	1.2k ¼ W, 1%	3	39k ¼ W, 5%
1	2.4k ¼ W, 1%	3	82k ¼ W, 5%
1	4.7k ¼ W, 5%	1	220k ¼ W, 5%
1	5.1k ¼ W, 1%	1	4.7 M ¼ W, 5%
2	5.1k ¼ W, 5%	1	1k Trimpot
1	10k ¼ W, 5%	1	10k Trimpot
2	50k Trimpot		
Capacitors			
3	43 pF Mica		Capacitors
2	100 pF Mica	3	*0.0047 μ F Mylar™
1	1000 pF Mica	1	*0.01 μ F Mylar
1	0.001 μ F	6	*0.022 μ F Mylar
1	0.01 μ F	2	*0.068 μ F Mylar
		1	*25 μ F Mylar
			Small Signal Diodes
		8	*1N914
			* Or equivalent.

cial units have one advantage in that they can be purchased and plugged into the wall and they are operational. The computerized system described takes a little more work, but it is extremely flexible and not subject to obsolescence as are its commercial counterparts. The results achieved with the system described here rivaled those of commercial counterparts.

Photo F is a typical color image, 128 pixels per line on 128 lines, 256 colors per pixel. Photo G is another color-SSTV image which shows the resolution of the display board on facial flesh tones. This type of image is the hardest type to display. This picture shows color contouring due to the 256 colors per pixel. Photo H is another color picture with computer-graphics overlays generated by software. The picture is the same as Photo G but reduced in size by one half. The colored image was



Photo H. A color-SSTV picture with graphics. This picture is the same as Photo G, but reduced in size by software and placed in the center of the image area. The graphics were generated by software and placed around the picture. The graphics and picture were all generated by the K6AEP SSTV 7.6 Revision 2 program.

moved to the center of the display screen and graphical characters of various colors

were distributed around the picture.

Better results can be

achieved with 32K of display memory, but photos were not presented in this article for this mode. The black and white images developed by this display density approach fast-scan TV quality.

More photos will be presented in Part II of the article, on the FAX application.

Obviously a project of this magnitude is not a one-person effort. Some of the people who contributed were Ron Adair K5HFT of Multimode Corporation, Bob Blackstock WB5MRC who helped with the display-board design, Larry Fritz AG8O of L. W. InterFace, and Bob Wilson WBØRTM of RTM Circuit Boards. ■

References

- ¹ Multimode Corp., PO Box 171171, Arlington TX 76016; (817)-572-3996.
- ² RTM Circuit Boards, 205 Elm Street, Van Horne IA 52346-0400.
- ³ L. W. InterFace, 9570 Kinsman Road, Novelty OH 44072.

here is the next generation Repeater

MARK 4CR

The **only** repeaters and controllers with REAL SPEECH!

No other repeaters or controllers match Mark 4 in capability and features. That's why Mark 4 is the performance leader at amateur and commercial repeater sites around the world. Only Mark 4 gives you Message Master™ real speech • voice readout of received signal strength, deviation, and frequency error • 4-channel receiver voting • clock time announcements and function control • 7-helical filter receiver • extensive phone patch functions. Unlike others, Mark 4 even includes power supply and a handsome cabinet.

Call or write for specifications on the repeater, controller, and receiver winners.

Create messages just by talking. Speak any phrases or words in any languages or dialect and *your own voice* is stored instantly in solid-state memory. Perfect for emergency warnings, club news bulletins, and DX alerts. Create unique ID and tail messages, and the ultimate in a real speech user mailbox — only with a Mark 4.



MICRO CONTROL SPECIALTIES

Division of Kendecom Inc.

23 Elm Park, Groveland, MA 01834 (617) 372-3442